

Final Exam: 2021/06/09, 10:30 AM – 12:00PM including preparation/submission.

Name: 김다영

Student ID: 12201856

54

Honor Code: Please write this honor code below with your signature either in Korean or in English.

“나는 정직하게 시험에 응할 것을 서약합니다.”

“By signing this pledge, I promise to adhere to exam requirements and maintain the highest level of ethical principles during the exam period.”

나는 정직하게 시험에 응할 것을 서약합니다.

Name/Student ID: 김다영 / 12201856

Date: 21.06.09

Signature: 김다영

Before the exam

- Camera should be on during the exam.
- Official student ID card is required for your identification.
- Official answer sheets (from I-Class) should be printed before the exam.

During the exam

- It is closed book test.
- You can use personal calculator.
- Chatting or discussion is NOT allowed.
- You need to turn on your ONE microphone during the exam.

After the exam

- Take photos (or scan) of your answer sheets and please check image quality.
- E-mail these photos to you and to instructor: mgk@inha.ac.kr within 5 mins.
- Upload a combined pdf file to I-Class (midterm section) within 10 mins.
- Submit original papers within a week (deadline: 06.18 Fri).

Question Number: 1

$$t > 0. \quad \bar{I}_b = -5e^{-50t} \text{ [mA]}$$

$$V_a(0) = -20$$

$$V_c(0) = -30$$

$$V_d(0) = 250.$$



$$\bar{I}_b = C \frac{dV}{dt}$$

$$V = \frac{1}{C} \int_{t_0}^t \bar{I}_b dt + V_b(0)$$

=

3
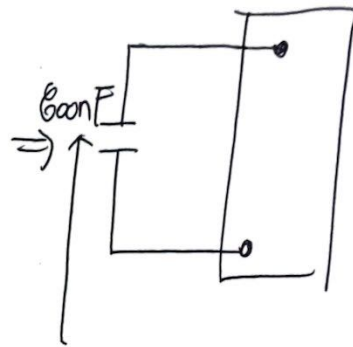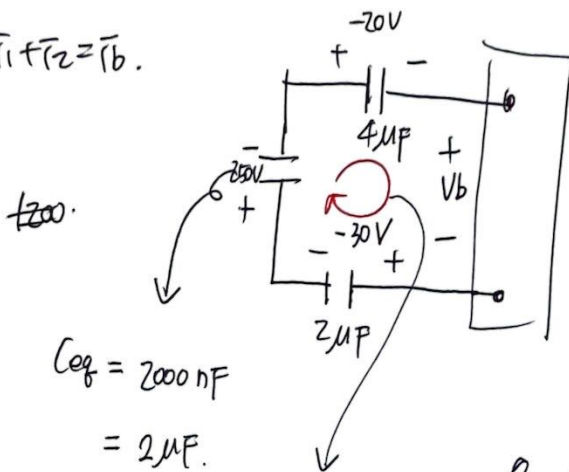
$$\textcircled{4}. \quad \bar{I}_1 + \bar{I}_2 = \bar{I}_b.$$



$$\bar{I}_b = C \frac{dV}{dt}.$$

$$250 - 20 + V_b - 30 = 0$$

$$V_b = -200 \text{ V.}$$

$$\frac{1}{2\mu\text{F}} + \frac{1}{2\mu\text{F}} + \frac{1}{4\mu\text{F}} = \frac{1}{C_{eq'}}$$

$$C_{eq'} = 0.8\mu\text{F}$$

1.5

$$\therefore V_b = \frac{1}{C} \int_{t_0}^t -5e^{-50t} dt + V_b(0)$$

$$= \frac{1}{0.8\mu} \int_0^t -5e^{-50t} dt - 200$$

$$= \frac{10^6}{0.8} \left[\frac{1}{50} e^{-50t} \right]_0^t - 200 = \frac{10^6}{0.8} \left(\frac{1}{50} e^{-50t} - \frac{1}{50} \right) - 200$$

$$= \frac{10^5}{0.8} (e^{-50t} - 1) - 200 =$$

$$= 125000e^{-50t} - 125200$$

$$\therefore i_1(t) = \bar{I}_b \cdot \frac{1200n}{1200n + 800n} = -3e^{-50t} \text{ mA}$$



$$\therefore i_2(t) = \bar{I}_b \cdot \frac{800n}{1200n + 800n} = -2e^{-50t} \text{ (mA)}$$

1.5


$$\therefore V_a = \frac{(2\mu\text{F} \parallel 2\mu\text{F})}{4\mu\text{F} + (2\mu\text{F} \parallel 2\mu\text{F})} V_b$$

Question Number: 2

①

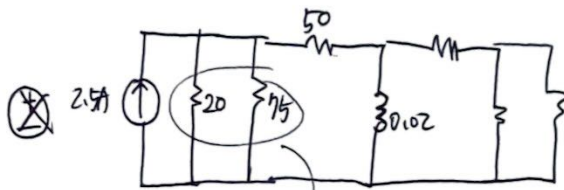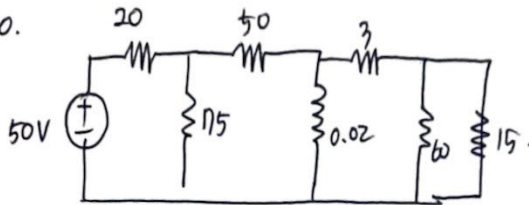
 $t < 0$.

0.02 H에 걸리는 전류. $\rightarrow 20 \parallel 75 = 15.19 \Omega$

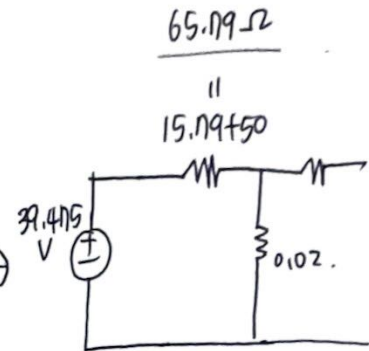 $t \geq 0$.


$$T(t) = C \frac{dV}{dt}$$

Question Number: 3

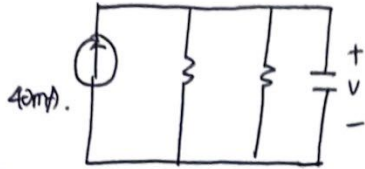
a) $t < 0$.

$$2.7k \parallel 3.3k = 1.485k$$

12

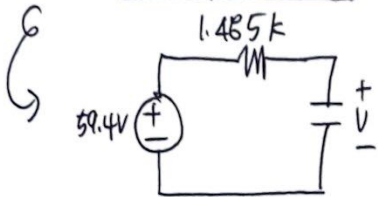


$$V_{C0} = 59.4V.$$

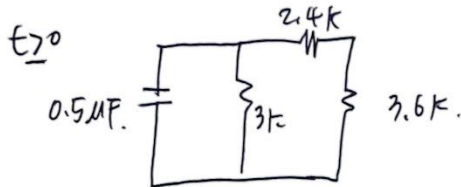

$$\tau = RC = 2k \cdot 0.5 \cdot 10^{-6} = 1ms.$$

$$= 10^{-3}s.$$

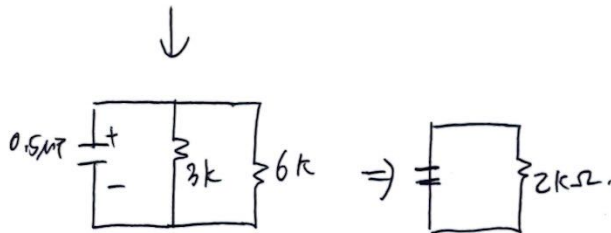

$$V(t) = V_0 e^{-\frac{t}{\tau}} = 59.4 e^{-1000t} [V].$$

7.5

$$b). \quad i(t) = \frac{C dV}{dt} = 0.5\mu \cdot \frac{d}{dt} (59.4 e^{-1000t})$$

$$= 0.5 \times 10^{-6} \cdot 59.4 (-1000) e^{-1000t}$$


$$= -29.7 \cdot 10^{-3} e^{-1000t}$$

$$\frac{3}{9} = \frac{1}{3}$$

5.5

by. 전류분배법칙.

$$-29.7 \cdot 10^{-3} e^{-1000t}$$




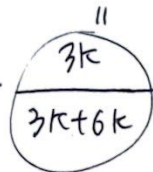


$$= \frac{3k}{3k + 6k} \cdot (-29.7 \cdot 10^{-3} e^{-1000t}) = -9.9 \cdot 10^{-3} e^{-1000t} A = i(t).$$


Question Number: 4

$t < 0$

a)

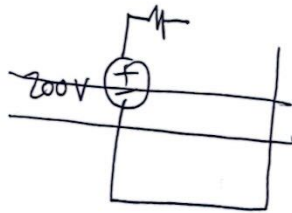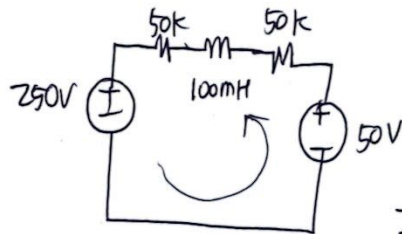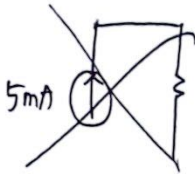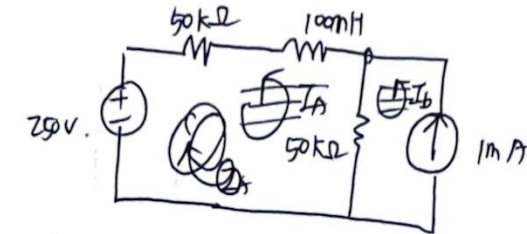


b).

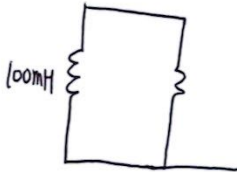

b).

$t > 0$


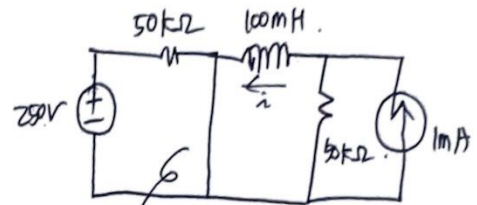


$R=0$ 이므로 250V 전압원에 의한 전류가 영향을 미치지 X.


$\therefore I_p = 1mA \cdot \left(\frac{250V}{1mA} \right) \cdot 2$

$$I_0 = \frac{200}{100k} = 2mA = i$$

Question Number: 5

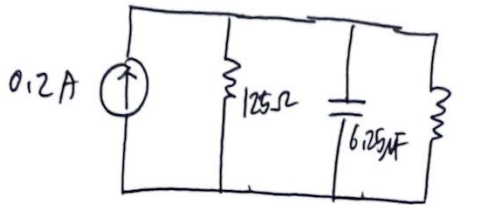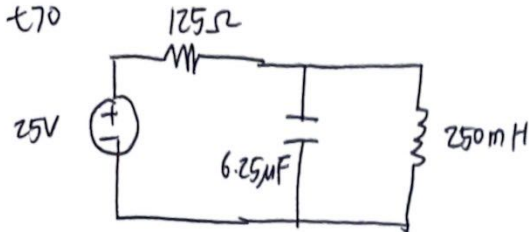

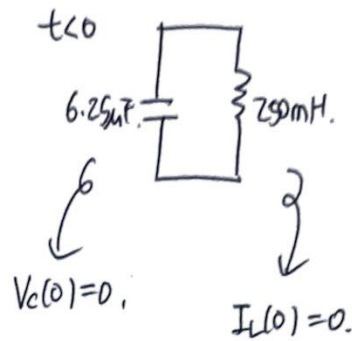RLC, ~~1st~~ 2nd Step. $\left(\frac{1}{L}\right) A$.
 \overline{I}



because, no energy stored!

$$R = 125 \Omega$$

$$C = 6.25 \cdot 10^{-6} \text{ F}$$

$$L = 250 \cdot 10^{-3} \text{ H}$$

$$\overline{I} = 0.2 \text{ [A]}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 125 \cdot 6.25 \cdot 10^{-6}} = 640$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{6.25 \times 250 \cdot 10^{-9}} = 800$$

$$\alpha^2 < \omega_0^2 \Rightarrow \text{underdamped!}$$

$$\omega_d = 480$$

$$\begin{aligned} \overline{I}_L(t) &= \overline{I}_p + B_1' e^{-640t} \cos 480t + B_2' e^{-640t} \sin 480t \\ &= 0.2 + B_1' e^{-640t} \cos 480t + B_2' e^{-640t} \sin 480t \end{aligned}$$

$$\overline{I}_L(0) = 0.2 + B_1' = 0 \quad B_1' = -0.2$$

Name/Student ID: 20210156

$$V_C(t) = 250 \cdot 10^{-3} \left(128 e^{-640t} \cos 480t + 96 e^{-640t} \sin 480t + 110.88 e^{-640t} \sin 480t - 128.16 e^{-640t} \cos 480t \right)$$

$$\begin{aligned} \overline{I}_C(t) &= \overline{I}_L(t) = 0.2 - 0.2 e^{-640t} \cos 480t + (-0.267) e^{-640t} \sin 480t \\ V_C(t) &= L \frac{d\overline{I}_L(t)}{dt} = 250 \cdot 10^{-3} \cdot \left\{ 0.2 \cdot 640 e^{-640t} \cos 480t + 0.2 e^{-640t} \sin 480t \right. \\ &\quad \left. + 0.267 e^{-640t} \cdot 640 \sin 480t + (-0.267) e^{-640t} \cos 480t \cdot 480 \right\} \end{aligned}$$

$$\frac{d\overline{I}_L(t)}{dt} = \frac{V_L}{L} = 0$$


$$= -640 B_1' + 480 B_2'$$

$$\frac{640 B_1'}{480} = B_2' = \frac{640}{480} (-0.2) = -0.267$$

Question Number: 6


9

t=0

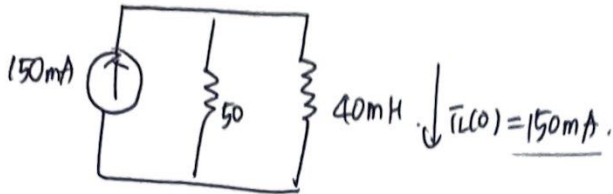

$$i_L(0) = 150 \cdot 10^{-3} [A]$$

t=20

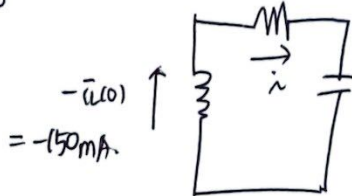

$$R = 20 \Omega$$

$$L = 40 \cdot 10^{-3} H$$

$$C = 400 \cdot 10^{-6} F$$

RLC회로. Natural. 7Hz.

$$\alpha = \frac{R}{2L} = \frac{20}{2 \cdot 40 \cdot 10^{-3}} = 250$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{40 \cdot 400 \cdot 10^{-9}} = 250^2$$

$$\alpha^2 = \omega_0^2 \quad \text{critically damped!}$$

$$i(t) = D_1 t e^{-250t} + D_2 e^{-250t}$$

$$\therefore i(t) = \underline{-37500t e^{-250t} - 150 e^{-250t}} [mA]$$

$$i(0) = D_2 = I_0 = -150mA$$

$$\frac{di(0^+)}{dt} = D_1 - 250D_2 = \frac{1}{L}(-V_R - V_C) = 0$$

$$D_1 = 250D_2 = 250 \cdot (-150) \cdot 10^{-3} = -37500 \cdot 10^{-3}$$

$$b_6 \quad N \quad I(t) \quad V(t)$$

$$S \quad V(t) \quad I_L(t)$$


$$Z_1 \quad N \quad I(t)$$

$$S \quad V_C(t)$$


9

Question Number: 11

8

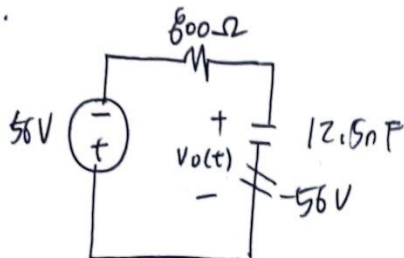 $t < 0$.

$$V_c(0) = -56V$$

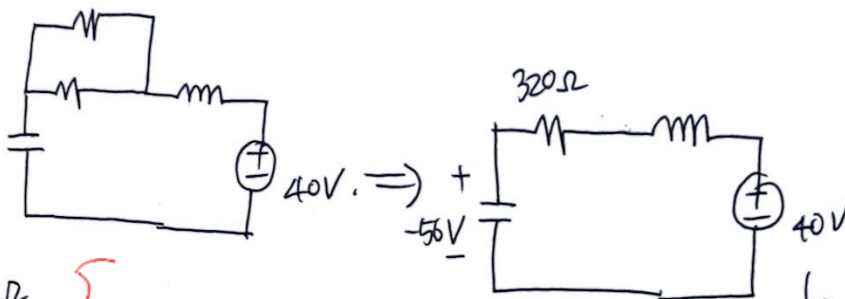 $t \geq 0$ 

$$R = 320\Omega$$

$$L = 0.5 \cdot 10^{-3} H$$

$$C = 12.5 \cdot 10^{-9} F$$

Step.

$$V_c(\infty) = 40V$$

$$V_c(0) = -56V$$

$$\alpha = \frac{R}{2L} = \frac{320}{2 \cdot 0.5 \cdot 10^{-3}} = 320000$$

$$\omega_0^2 = \frac{1}{L C} = \frac{1}{0.5 \times 12.5 \times 10^{-12}} = 1.6 \times 10^{11} = 400000^2$$

$$\omega_0^2 - \alpha^2 > 0 \quad \text{underdamped!}$$

$$\omega_d = 240000 \quad \alpha = 320000$$

$$\therefore V_c(t) = 40 - 96e^{-320000t} \cos 240000t - 128e^{-320000t} \sin 240000t$$

$$V_c(t) = 40 + B_1' e^{-320000t} \cos 240000t + B_2' e^{-320000t} \sin 240000t$$

$$V_c(0) = 40 + B_1' = -56$$

$$B_1' = -96V$$

$$\frac{dV_c(t)}{dt} = \frac{I_C}{C}$$

$$\frac{dV_c(t)}{dt} = \frac{I_C}{C} = -320000 B_1' + 240000 B_2' = 0$$

$$B_2' = \frac{320000}{240000} B_1' = -128$$