

HW#1 Solution**Chapter 1.****[Problem 1] Text page 48, Problem 1.9**

P 1.9 [a] First we use Eq. (1.2) to relate current and charge:

$$i = \frac{dq}{dt} = 40te^{-500t}.$$

Therefore, $dq = 40te^{-500t} dt$.

To find the charge, we can integrate both sides of the last equation. Note that we substitute x for q on the left side of the integral, and y for t on the right side of the integral:

$$\int_{q(0)}^{q(t)} dx = 40 \int_0^t ye^{-500y} dy.$$

We solve the integral and make the substitutions for the limits of the integral:

$$\begin{aligned} q(t) - q(0) &= 40 \frac{e^{-500y}}{(-500)^2} (-500y - 1) \Big|_0^t \\ &= 160 \times 10^{-6} e^{-500t} (-500t - 1) + 160 \times 10^{-6} \\ &= 160 \times 10^{-6} (1 - 500te^{-500t} - e^{-500t}). \end{aligned}$$

But $q(0) = 0$ by hypothesis, so

$$q(t) = 160(1 - 500te^{-500t} - e^{-500t}) \mu\text{C}.$$

$$[b] \quad q(0.001) = (160)[1 - 500(0.001)e^{-500(0.001)} - e^{-500(0.001)}] = 14.4 \mu\text{C}.$$

[Problem 2] Text page 49, Problem 1.14

P 1.14 Assume we are standing at box A looking toward box B. Use the passive sign convention to get $p = vi$, since the current i is flowing into the + terminal of the voltage v . Now we just substitute the values for v and i into the equation for power. Remember that if the power is positive, B is absorbing power, so the power must be flowing from A to B. If the power is negative, B is generating power so the power must be flowing from B to A.

- [a] $p = (40)(8) = 320 \text{ W}$ 320 W from A to B;
- [b] $p = (-10)(-2) = 20 \text{ W}$ 20 W from A to B;
- [c] $p = (-50)(2) = -100 \text{ W}$ 100 W from B to A;
- [d] $p = (20)(-10) = -200 \text{ W}$ 200 W from B to A.

[Problem 3] Text page 49, Problem 1.18

P 1.18 [a] $p = vi = (3e^{-50t})(0.005e^{-50t}) = 0.015e^{-100t}$ W


$$p(0.005) = 0.015e^{-100(0.005)} = 0.015e^{-0.5} = 9.1 \text{ mW}.$$

[b] $w_{\text{total}} = \int_0^{\infty} p(x) dx = \int_0^{\infty} 0.015e^{-100x} dx = 0.015 \frac{e^{-100x}}{e^{-100}} \bigg|_0^{\infty}$
 $= -0.00015(e^{-\infty} - e^0) = 0.00015 = 0.15 \text{ mJ}.$

Chapter 2.

[Problem 4] Text page 81, Problem 2.18

P 2.18

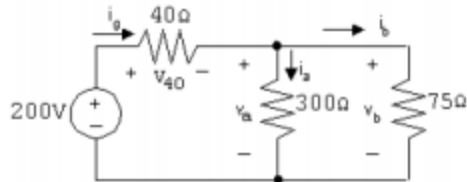

- [a] Write a KVL equation clockwise around the right loop, starting below the 300Ω resistor:

$$-v_a + v_b = 0 \quad \text{so} \quad v_a = v_b.$$

Using Ohm's law,

$$v_a = 300i_a \quad \text{and} \quad v_b = 75i_b.$$

Substituting,

$$300i_a = 75i_b \quad \text{so} \quad i_b = 4i_a.$$

Write a KCL equation at the top middle node, summing the currents leaving:

$$-i_g + i_a + i_b = 0 \quad \text{so} \quad i_g = i_a + i_b = i_a + 4i_a = 5i_a.$$

Write a KVL equation clockwise around the left loop, starting below the voltage source:

$$-200 \text{ V} + v_{40} + v_a = 0.$$

From Ohm's law,

$$v_{40} = 40i_g \quad \text{and} \quad v_a = 300i_a.$$

Substituting,

$$-200 \text{ V} + 40i_g + 300i_a = 0$$

Substituting for i_g :

$$-200 \text{ V} + 40(5i_a) + 300i_a = -200 \text{ V} + 200i_a + 300i_a = -200 \text{ V} + 500i_a = 0.$$

Thus,

$$500i_a = 200 \text{ V} \quad \text{so} \quad i_a = \frac{200 \text{ V}}{500} = 0.4 \text{ A}.$$

[b] From part (a), $i_b = 4i_a = 4(0.4 \text{ A}) = 1.6 \text{ A}$.

[c] From the circuit, $v_o = 75 \Omega(i_b) = 75 \Omega(1.6 \text{ A}) = 120 \text{ V}$.

[d] Use the formula $p_R = Ri_R^2$ to calculate the power absorbed by each resistor:

$$p_{40\Omega} = i_g^2(40 \Omega) = (5i_a)^2(40 \Omega) = [5(0.4)]^2(40 \Omega) = (2)^2(40 \Omega) = 160 \text{ W};$$

$$p_{300\Omega} = i_a^2(300 \Omega) = (0.4)^2(300 \Omega) = 48 \text{ W};$$

$$p_{75\Omega} = i_b^2(75 \Omega) = (4i_a)^2(75 \Omega) = [4(0.4)]^2(75 \Omega) = (1.6)^2(75 \Omega) = 192 \text{ W}.$$

[e] Using the passive sign convention,

$$\begin{aligned} p_{\text{source}} &= -(200 \text{ V})i_g = -(200 \text{ V})(5i_a) = -(200 \text{ V})[5(0.4 \text{ A})] \\ &= -(200 \text{ V})(2 \text{ A}) = -400 \text{ W}. \end{aligned}$$


Thus the voltage source delivers 400 W of power to the circuit. Check:

$$\sum P_{\text{dis}} = 160 + 48 + 192 = 400 \text{ W};$$

$$\sum P_{\text{del}} = 400 \text{ W}.$$

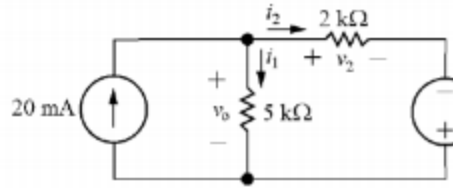[Problem 5] Text page 81, Problem 2.20

P 2.20 Label the unknown resistor currents and voltages:



[a] KCL at the top node: $0.02 = i_1 + i_2$;

KVL around the right loop: $-v_o + v_2 - 5 = 0$.

Use Ohm's law to write the resistor voltages in the previous equation in terms of the resistor currents:

$$-5000i_1 + 2000i_2 - 5 = 0 \quad \rightarrow \quad -5000i_1 + 2000i_2 = 5.$$

Multiply the KCL equation by -2000 and add it to the KVL equation to eliminate i_2 :

$$-2000(i_1 + i_2) + (-5000i_1 + 2000i_2) = -2000(0.02) + 5 \quad \rightarrow \quad -7000i_1 = -35.$$

Solving,

$$i_1 = \frac{-35}{-7000} = 0.005 = 5 \text{ mA}.$$

Therefore,

$$v_o = Ri_1 = (5000)(0.005) = 25 \text{ V}.$$

[b] $p_{20\text{mA}} = -(0.02)v_o = -(0.02)(25) = -0.5 \text{ W}$;

$$i_2 = 0.02 - i_1 = 0.02 - 0.005 = 0.015 \text{ A};$$

$$p_{5\text{V}} = -(5)i_2 = -(5)(0.015) = -0.075 \text{ W};$$

$$p_{5\text{k}} = 5000i_1^2 = 5000(0.005)^2 = 0.125 \text{ W};$$


$$p_{2\text{k}} = 2000i_2^2 = 2000(0.015)^2 = 0.45 \text{ W};$$

$$p_{\text{total}} = p_{20\text{mA}} + p_{5\text{V}} + p_{5\text{k}} + p_{2\text{k}} = -0.5 - 0.075 + 0.125 + 0.45 = 0.$$

Thus the power in the circuit balances.

[Problem 6] Text page 82, Problem 2.26

P 2.26 [a]

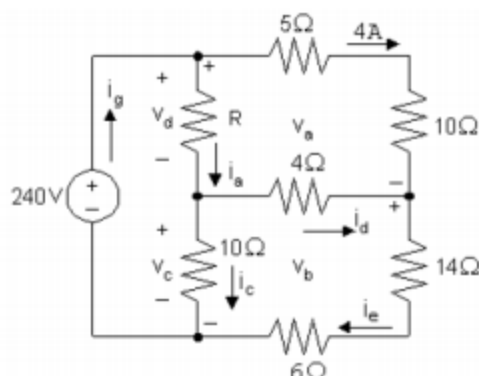


$$\begin{aligned}
 v_a &= (5 + 10)(4) = 60 \text{ V}; \\
 -240 + v_a + v_b &= 0 \quad \text{so} \quad v_b = 240 - v_a = 240 - 60 = 180 \text{ V}; \\
 i_e &= v_b / (14 + 6) = 180 / 20 = 9 \text{ A}; \\
 i_d &= i_e - 4 = 9 - 4 = 5 \text{ A}; \\
 v_c &= 4i_d + v_b = 4(5) + 180 = 200 \text{ V}; \\
 i_c &= v_c / 10 = 200 / 10 = 20 \text{ A}; \\
 v_d &= 240 - v_c = 240 - 200 = 40 \text{ V}; \\
 i_a &= i_d + i_c = 5 + 20 = 25 \text{ A}; \\
 R &= v_d / i_a = 40 / 25 = 1.6 \Omega.
 \end{aligned}$$

[b] $i_g = i_a + 4 = 25 + 4 = 29 \text{ A};$
 $p_g (\text{supplied}) = (240)(29) = 6960 \text{ W}.$

[Problem 7] Text page 83, Problem 2.35

P 2.35 [a] $i_o = 0$ because no current can exist in a single conductor connecting two parts of a circuit.

[b]

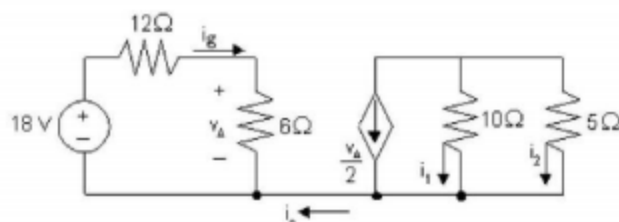

$$\begin{aligned}
 18 &= (12 + 6)i_g & i_g &= 1 \text{ A} \\
 v_\Delta &= 6i_g = 6 \text{ V} & v_\Delta/2 &= 3 \text{ A} \\
 10i_1 &= 5i_2 & \text{so} & \quad i_1 + 2i_1 = -3 \quad \text{A; therefore} \quad i_1 = -1 \text{ A.}
 \end{aligned}$$

[c] $i_2 = 2i_1 = -2 \text{ A}.$