
Engineering Circuits Analysis (ICE2002)

Chapter 6. Inductance, Capacitance, and Mutual Inductance - Part1/2/3

Contents

- The inductor
- The capacitor
- Series-Parallel Combinations of Inductance and Capacitance
- Mutual Inductance (skip)

Circuit Elements


Voltage sources



Voltage & current sources




Resistors

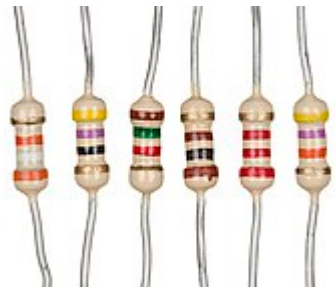

Capacitors



Inductors

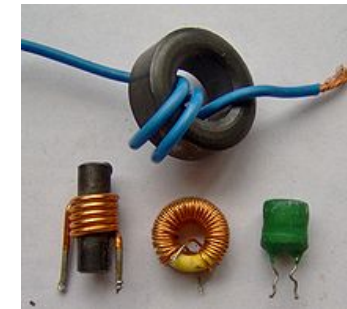

Circuit Elements

■ 5 ideal basic circuit elements

- Voltage source
- Current source




Active elements,
capable of generating electric energy

- Resistor
- Inductor
- Capacitor





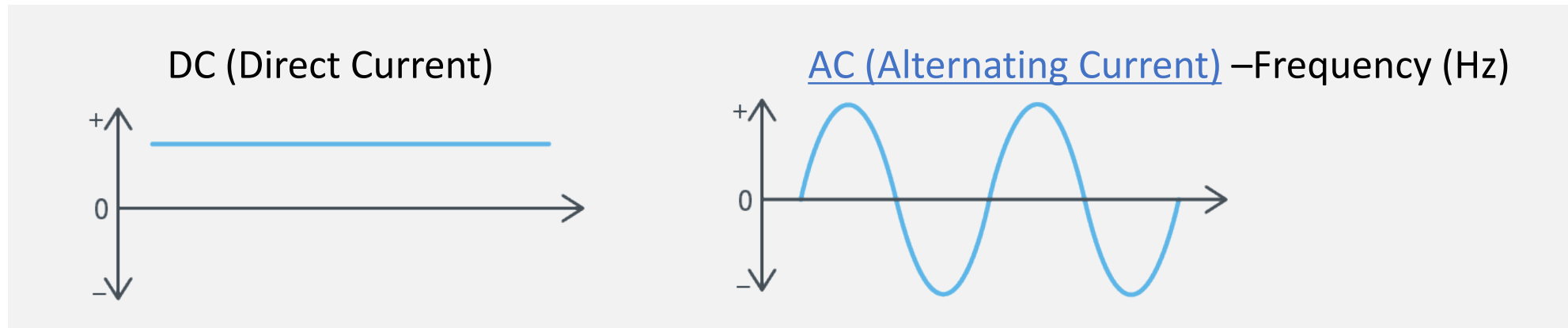Passive elements ,
incapable of generating electric energy



In Chapter 6,

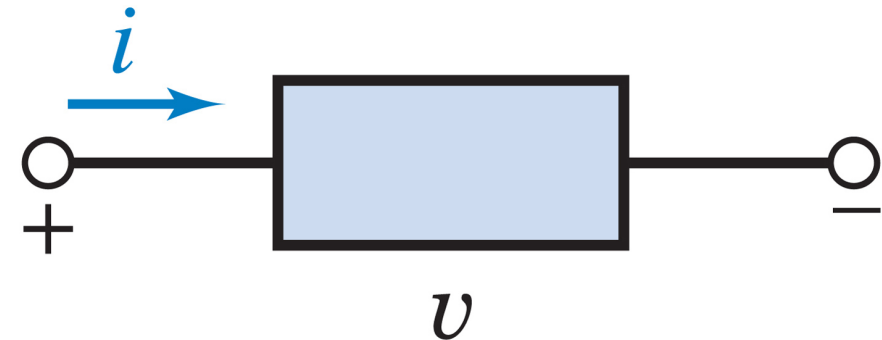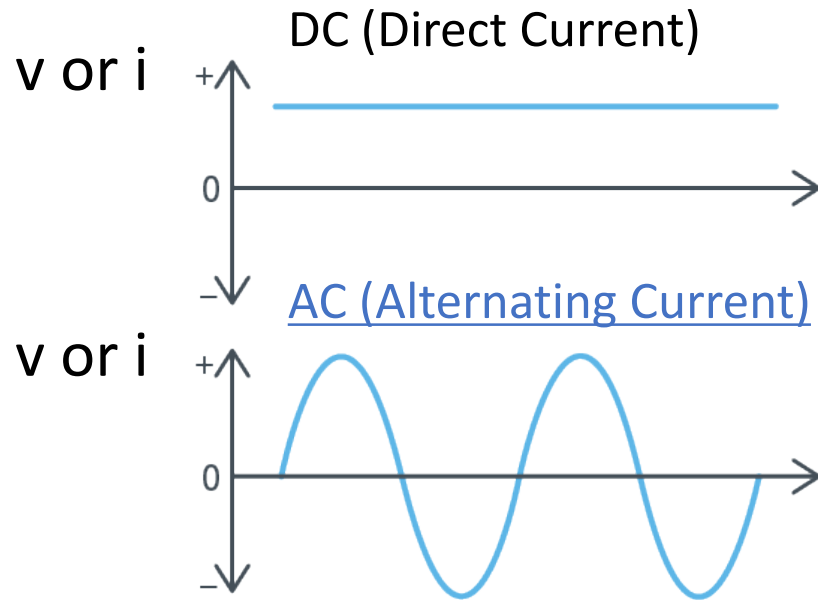- AC voltage sources, current sources, and inductors/capacitors can be described by plotting the voltage (v)/ current (i) as a function of current (i)/ voltage (v).




Review Chapter 2: Resistor and Ohm's Law

- **Ohm's law** establishes the proportionality of voltage and current in a resistor. It states that the voltage across a resistor is directly proportional to the current i flowing through the resistor.

$$v = Ri$$




where

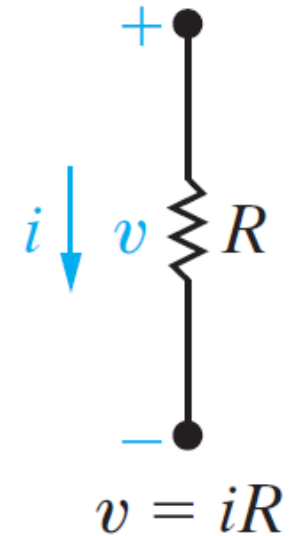v = the voltage in volts,
 i = the current in amperes,
 R = the resistance in ohms.



Inductor

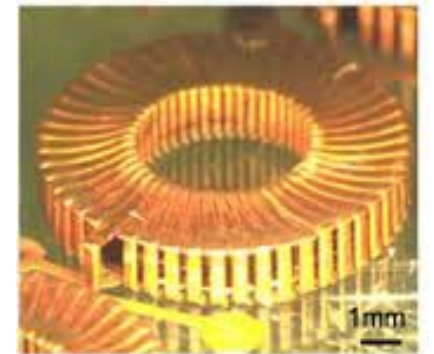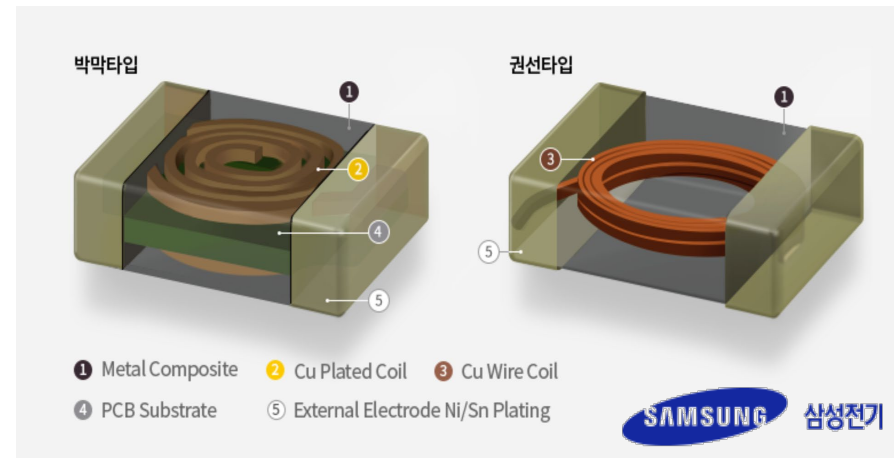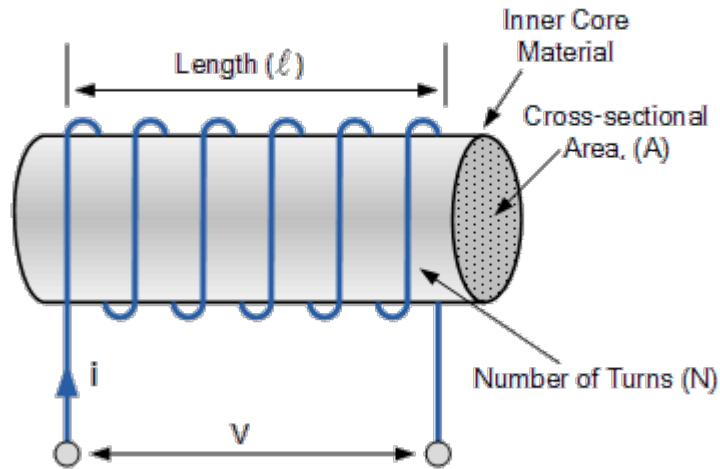
- An inductor is a **passive element** designed to **store energy in its magnetic field**.
- It is **a coil of wire** wound around supporting magnetic/or non-magnetic core material.




Ref) <https://www.electronics-tutorials.ws/inductor/inductor.html>

Inductor

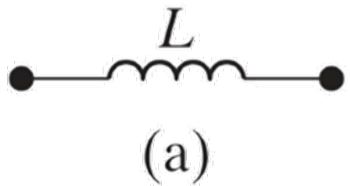- Inductance is a linear circuit parameter that relates the voltage induced by a time-varying magnetic field to the current producing the field.



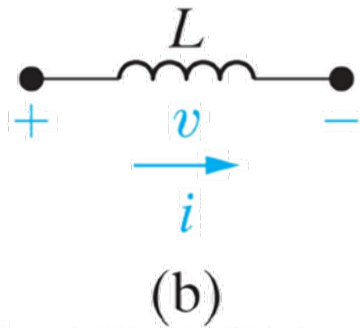
The graphic symbol for an inductor with an inductance of henrys [H].



Assigning reference voltage and current to the inductor following the passive sign convention.


$$v = L \frac{di}{dt}$$

Where
 v is measured in volts [V], L in henrys [H],
 i in amperes [A], and t in seconds [s].

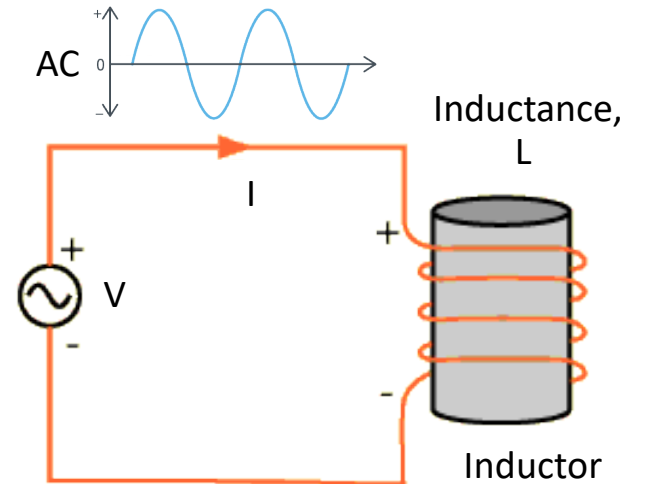

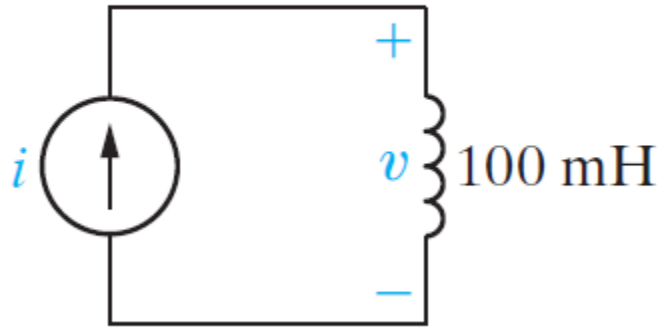
Example 6.1

Q. The independent current source in the circuit generates the pulse current.




$$i = 0, \quad t < 0$$
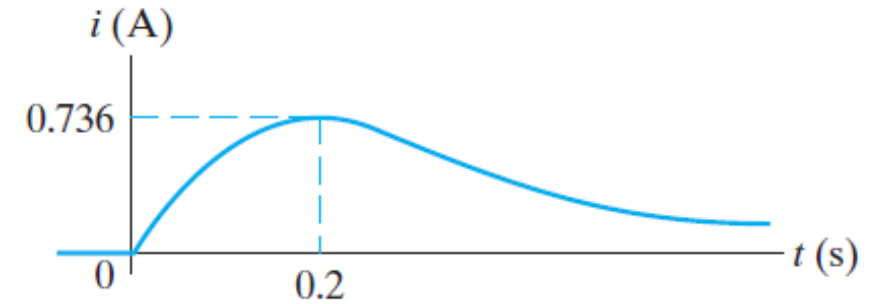
$$i = 10te^{-5t} \text{ A}, \quad t > 0$$




Current waveform

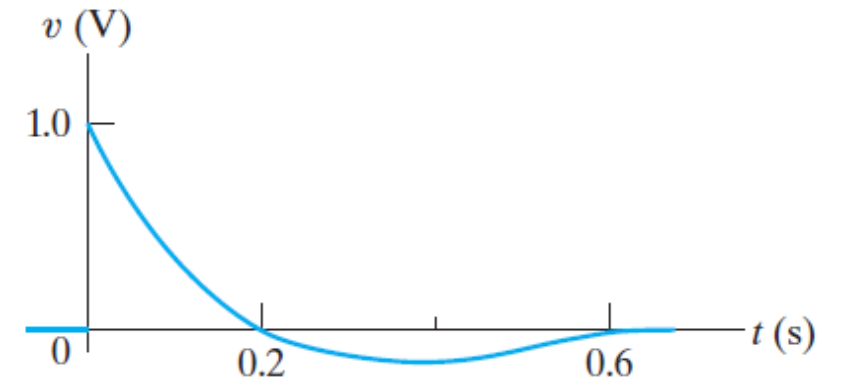

Voltage waveform

Voltage, Current, Power, Energy in an Inductor

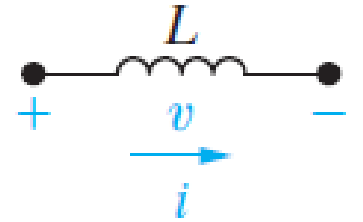- Inductor i (current) - v (voltage) equation



$$v = L \frac{di}{dt}$$

where

v is measured in volts [V], L in henrys [H],
 i in amperes [A], and t in seconds [s].


$$i(t) = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$$

where

$i(t_0)$ is the value of the inductor current at the time when we initiate the integration, namely, t_0 .

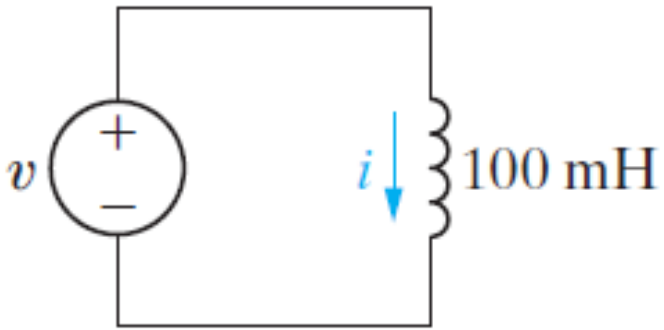
Example 6.2

Q. The independent voltage source in the circuit below generates the voltage pulse.




$$v = 0, \quad t < 0$$
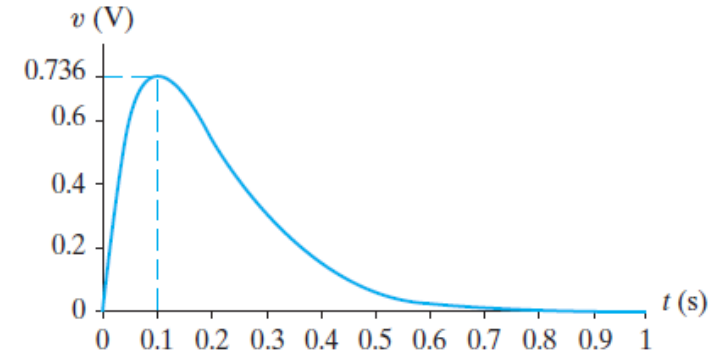
$$v = 20te^{-10t}\text{ V}, \quad t > 0$$




Voltage waveform

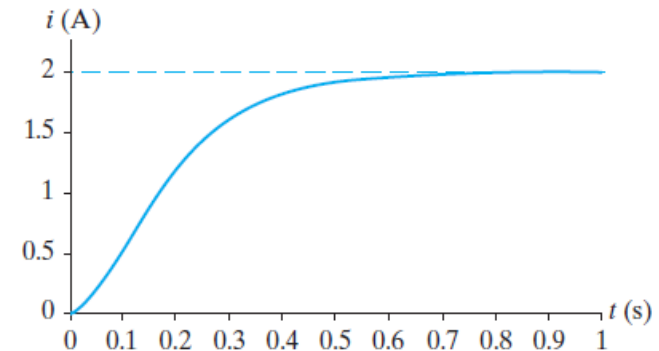


Current waveform

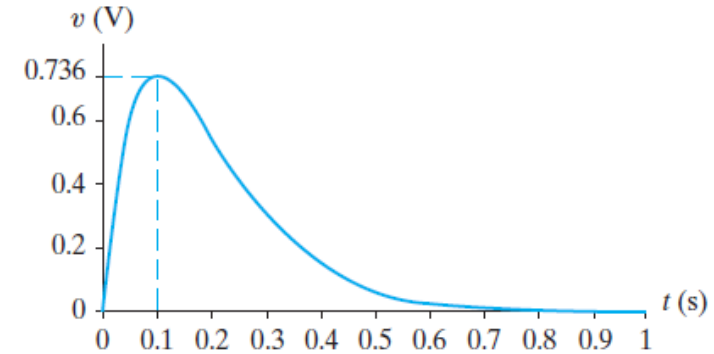Example 6.2

Q. The independent voltage source in the circuit below generates the voltage pulse.



Voltage waveform

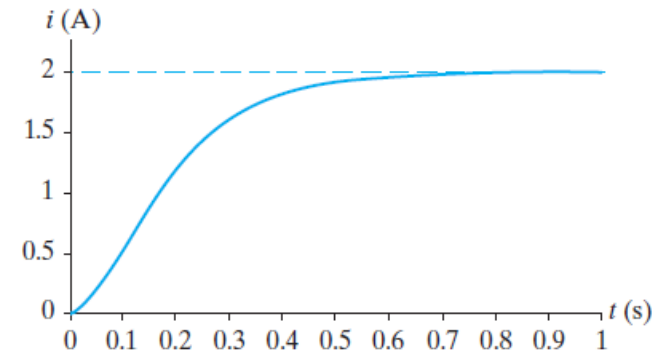

Current waveform


Voltage, Current, Power, Energy in an Inductor

- Power (P) and Energy (w) in an Inductor

$$P = \left(L \frac{di}{dt} \right) i \quad [W]$$


$$P = v \left(\frac{1}{L} \int_{t_0}^t v d\tau + i(t_0) \right) \quad [W]$$

$$w = \frac{1}{2} L i^2 \quad [J]$$

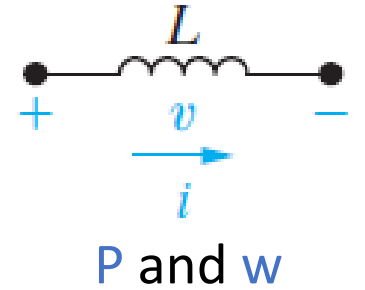

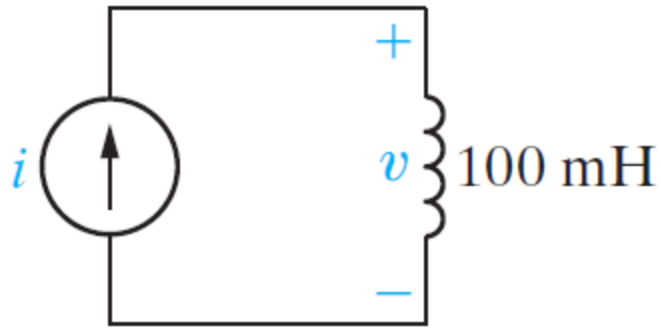
Example 6.3

Q. Find i , v , P and w of the circuit below




$$i = 0, \quad t < 0$$
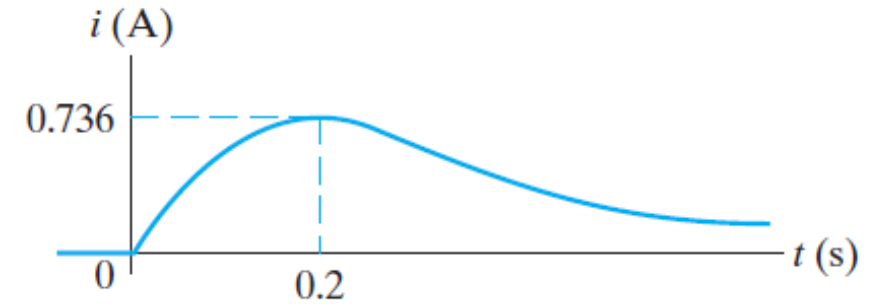
$$i = 10te^{-5t} \text{ A}, \quad t > 0$$





Current waveform

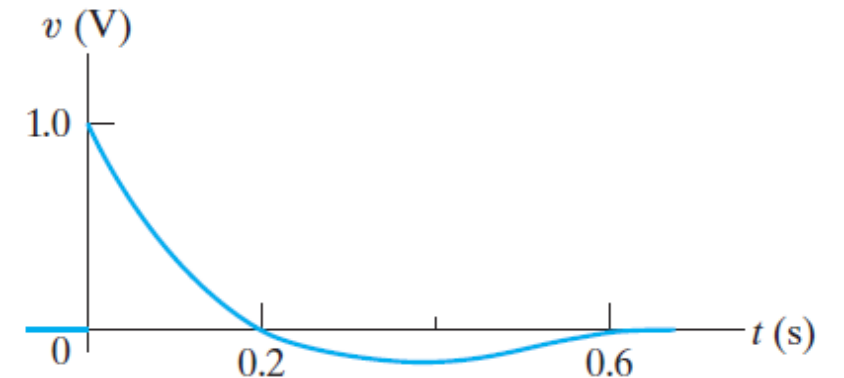

Voltage waveform

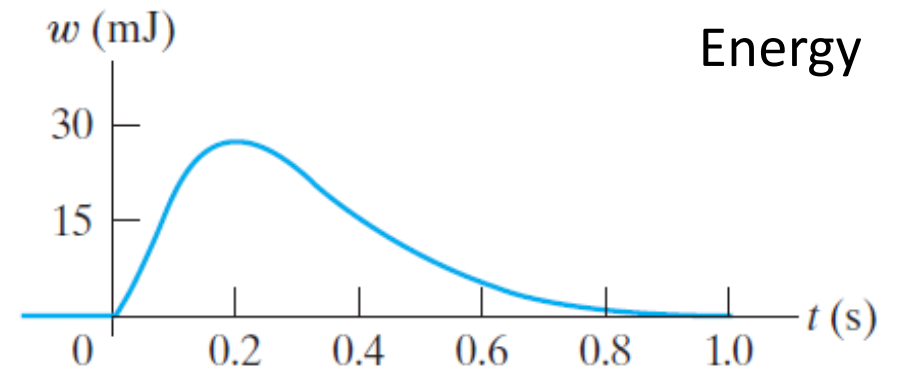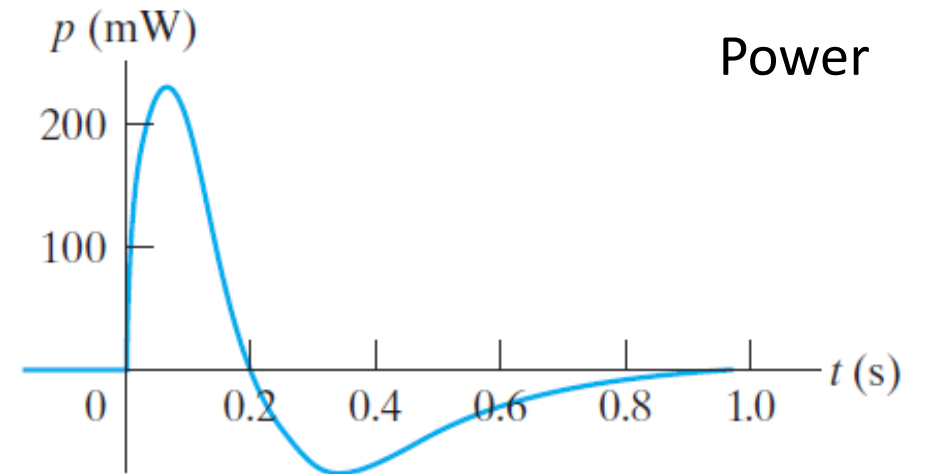
Example 6.3

Q. Find i , v , P and w of the circuit below



Capacitor

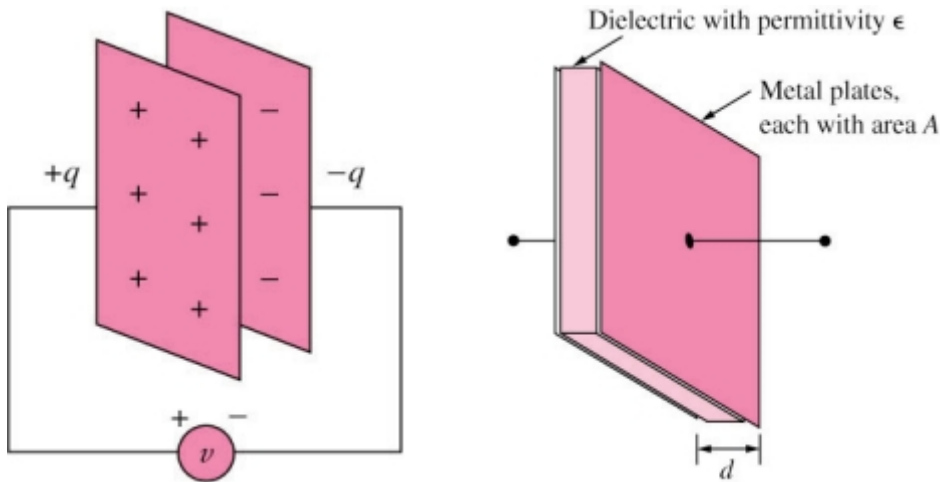- A capacitor is a passive element designed to store energy in its electric field.
- It consists of two conducting plates separated by an insulator (or dielectric).




$$q = C v \quad \text{and} \quad C = \frac{\epsilon A}{d}$$


- where
 - ϵ is the permittivity of the dielectric material between the plates,
 - A is the surface area of each plate,
 - d is the distance between the plates.
- Unit: F, pF (10^{-12}), nF (10^{-9}), and μF (10^{-6})

Capacitor

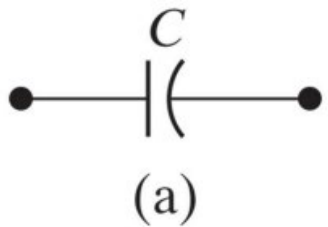- Capacitance is a linear circuit parameter that relates the current induced by a time-varying electric field to the voltage producing the field.



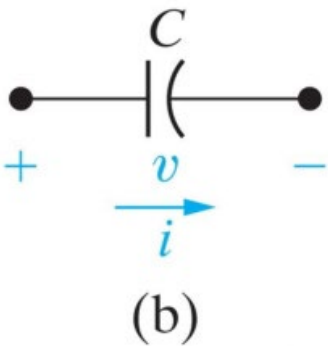
The graphic symbol for a capacitor with a capacitance of farads [F].



Assigning reference voltage and current to the capacitor, following the passive sign convention.


$$i = C \frac{dv}{dt}$$

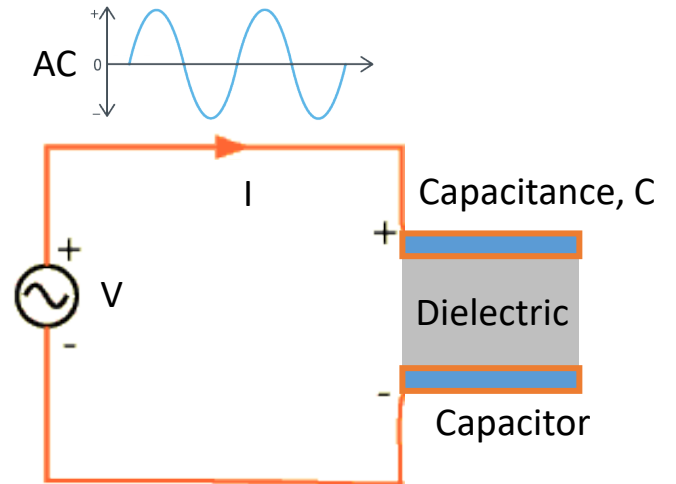where
 i in amperes [A], C in farads [F],
 v is measured in volts [V],
and t in seconds [s].



Voltage, Current, Power, Energy in a Capacitor

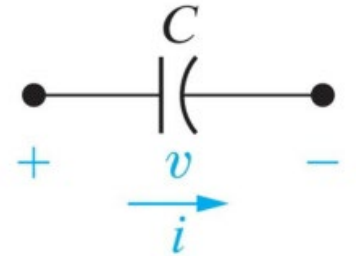- Capacitor i (current) - v (voltage) equation



$$i = C \frac{dv}{dt}$$

where
 i in amperes [A], C in farads [F],
 v is measured in volts [V],
and t in seconds [s].

$$v(t) = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$$

where
 $v(t_0)$ is the value of the capacitor voltage at the
time when we initiate the integration, namely, t_0 .


Voltage, Current, Power, Energy in an Inductor

- Power (P) and Energy (w) in an Inductor

$$P = v \left(C \frac{dv}{dt} \right) [W]$$

$$P = \left(\frac{1}{C} \int_{t_0}^t i d\tau + v(t_0) \right) i [W]$$

$$w = \frac{1}{2} C v^2 [J]$$

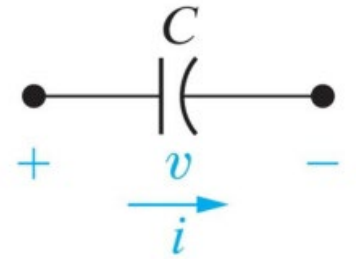

P and w



Example 6.4

Q. The voltage across the terminals of a $0.5 \mu\text{F}$ capacitor is:

$$= 0[V] \quad t \leq 0s$$

$$v(t) = 4t[V] \quad 0s \leq t \leq 1s$$

$$= 4e^{-(t-1)}[V] \quad t \geq 1s$$

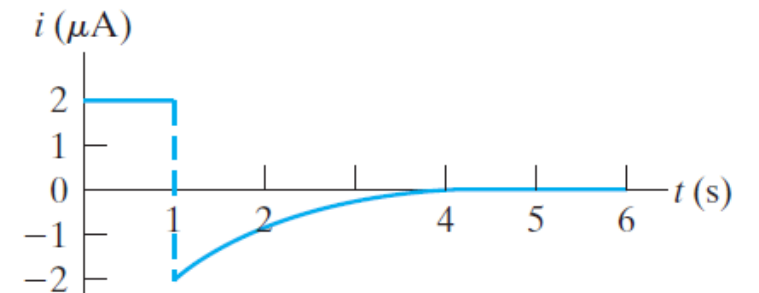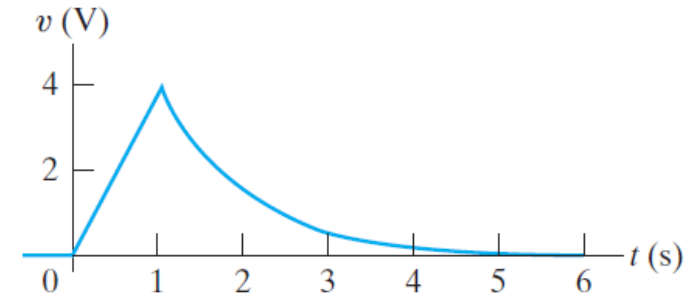


Example 6.4

Q. The voltage across the terminals of a $0.5 \mu\text{F}$ capacitor is:

$$= 0[V] \quad t \leq 0s$$

$$v(t) = 4t[V] \quad 0s \leq t \leq 1s$$

$$= 4e^{-(t-1)}[V] \quad t \geq 1s$$

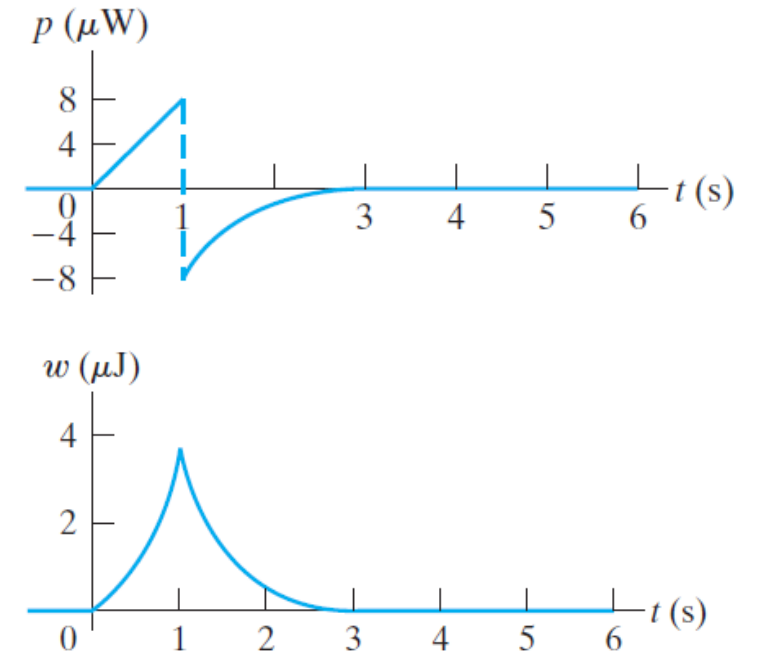

Example 6.4



Q. The current across the terminals of a $0.2 \mu\text{F}$ capacitor is:

$$= 0[A] \quad t \leq 0$$

$$i(t) = 5000t[A] \quad 0 \leq t \leq 20\mu\text{s}$$

$$= 0.2 - 5000t[A] \quad 20\mu\text{s} \leq t \leq 40\mu\text{s}$$

$$= 0[A] \quad t \geq 40\mu\text{s}$$

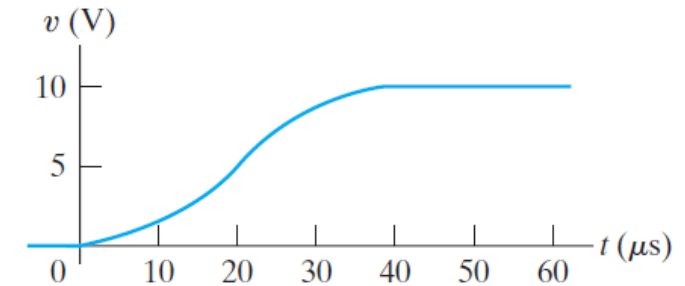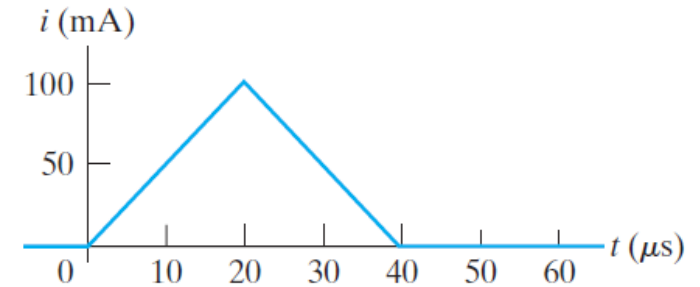

Example 6.4



Q. The current across the terminals of a $0.2 \mu\text{F}$ capacitor is:

$$= 0[A] \quad t \leq 0$$

$$i(t) = 5000t[A] \quad 0 \leq t \leq 20\mu\text{s}$$


$$= 0.2 - 5000t[A] \quad 20\mu\text{s} \leq t \leq 40\mu\text{s}$$

$$= 0[A] \quad t \geq 40\mu\text{s}$$

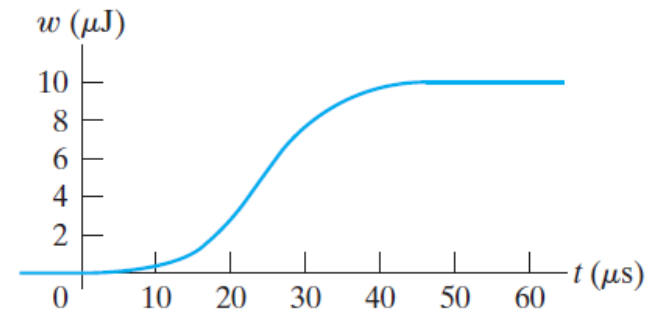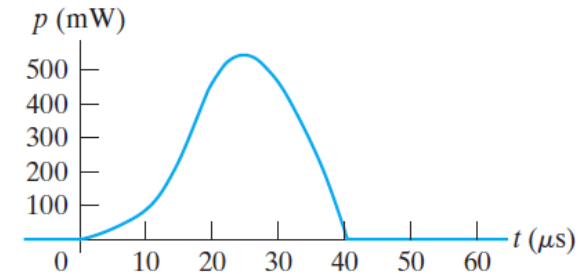

V, I, P, W in an Inductor

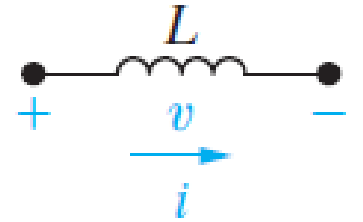- Inductor i (current) - v (voltage) equation



$$v = L \frac{di}{dt}$$

where

v is measured in volts [V], L in henrys [H],
 i in amperes [A], and t in seconds [s].

$$i(t) = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$$

where

$i(t_0)$ is the value of the inductor current at the time when we initiate the integration, namely, t_0 .


V, I, P, W in an Inductor

- Power (P) and Energy (w) in an Inductor

$$P = \left(L \frac{di}{dt} \right) i \quad [W]$$

$$P = v \left(\frac{1}{L} \int_{t_0}^t v d\tau + i(t_0) \right) \quad [W]$$

$$w = \frac{1}{2} L i^2 \quad [J]$$

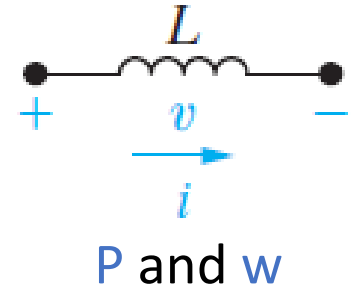


V, I, P, W in a Capacitor

- Capacitor i (current) - v (voltage) equation

$$i = C \frac{dv}{dt}$$

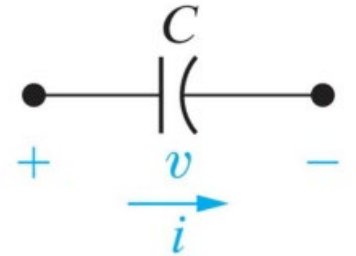where
 i in amperes [A], C in farads [F],
 v is measured in volts [V],
and t in seconds [s].



$$v(t) = \frac{1}{C} \int_{t_0}^t i dt + v(t_0)$$

where
 $v(t_0)$ is the value of the capacitor voltage at the time when we initiate the integration, namely, t_0 .


V, I, P, W in a Capacitor

- Power (P) and Energy (w) in a capacitor

$$P = v \left(C \frac{dv}{dt} \right) \quad [W]$$

$$P = \left(\frac{1}{C} \int_{t_0}^t i d\tau + v(t_0) \right) i \quad [W]$$

$$w = \frac{1}{2} C v^2 \quad [J]$$

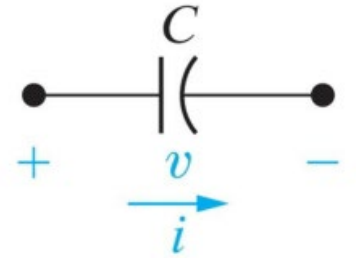


P and w


Series-Parallel Combinations of L and C

- Series-parallel combinations of inductors or capacitors can be reduced to a single inductor or capacitor.


Inductors in
series and parallel

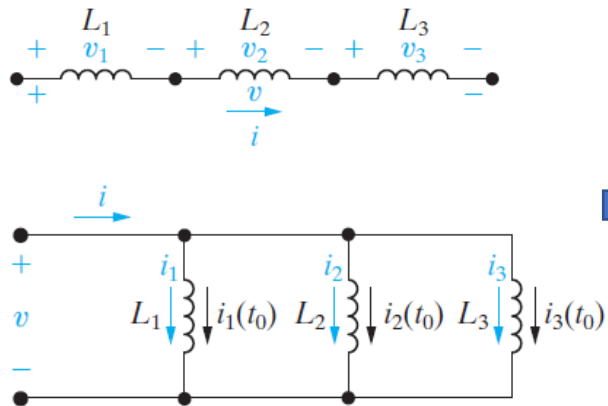


Equivalent inductor

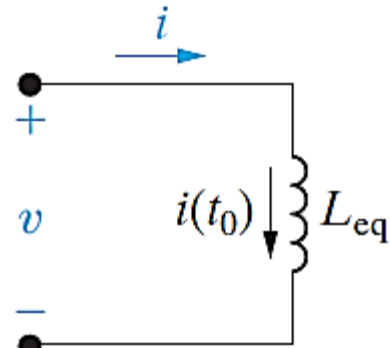

Capacitors in
series and parallel

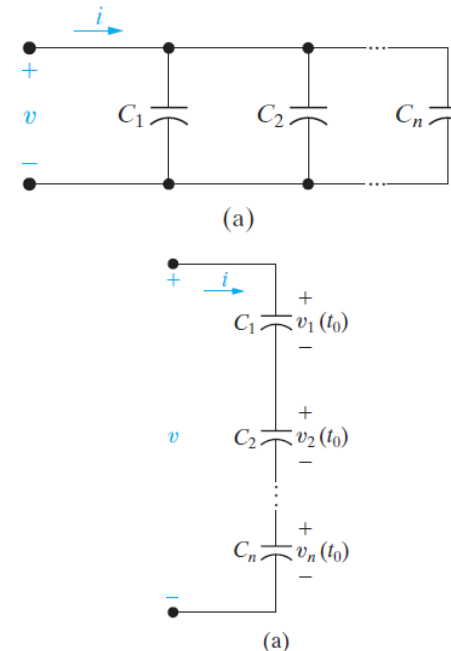


Equivalent capacitor

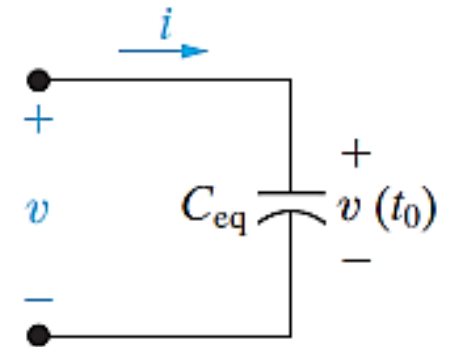

Inductors in Series and Parallel


Inductors in series

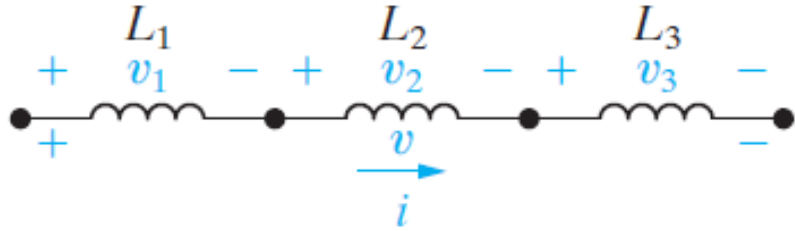

$$v = v_1 + v_2 + v_3$$

$$v_1 = L_1 \frac{di}{dt} \quad v_2 = L_2 \frac{di}{dt} \quad v_3 = L_3 \frac{di}{dt}$$


Combining inductors in series

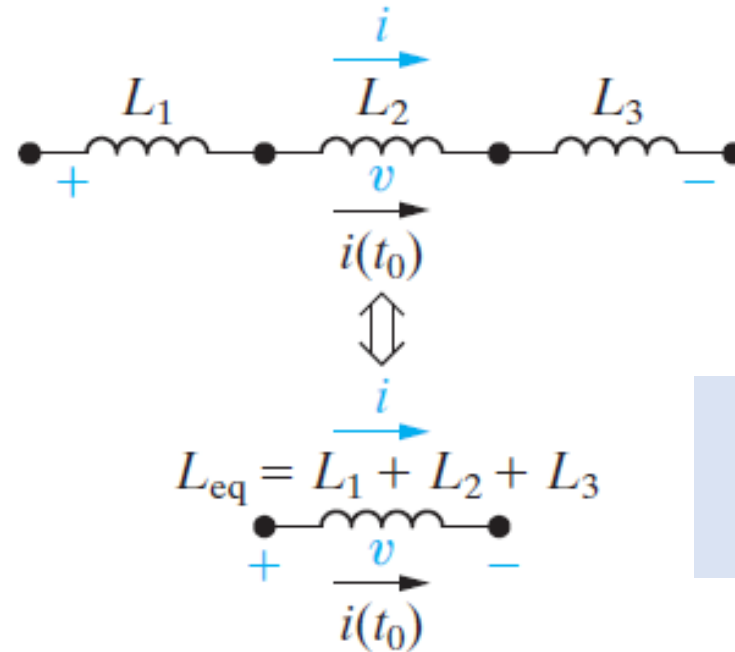

$$L_{eq} = \sum_{i=1}^n L_i$$

Inductors in Series and Parallel

Inductors in parallel

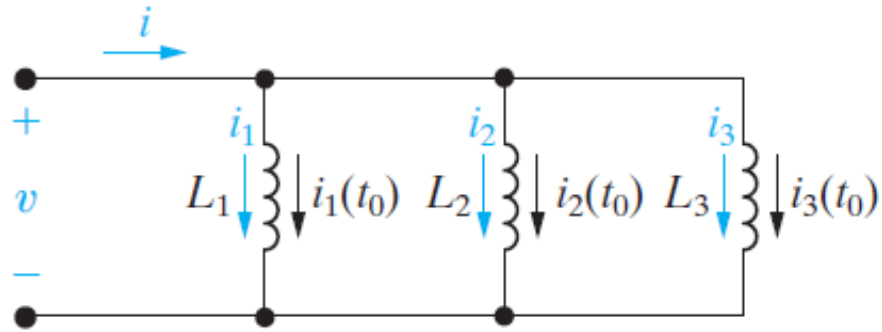


$$i = i_1 + i_2 + i_3$$

$$i_1 = \frac{1}{L_1} \int_{t_0}^t v dt + i_1(t_0)$$

$$i_2 = \frac{1}{L_2} \int_{t_0}^t v dt + i_2(t_0)$$

$$i_3 = \frac{1}{L_3} \int_{t_0}^t v dt + i_3(t_0)$$

Combining inductors in parallel

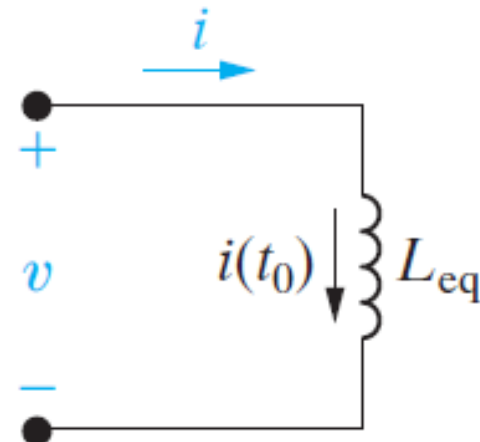

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$


$$i(t_0) = i_1(t_0) + i_2(t_0) + i_3(t_0)$$

$$\frac{1}{L_{eq}} = \sum_{i=1}^n \frac{1}{L_i}$$

$$i(t_0) = \sum_{j=1}^n i_j(t_0)$$

Inductors in Series and Parallel

Example

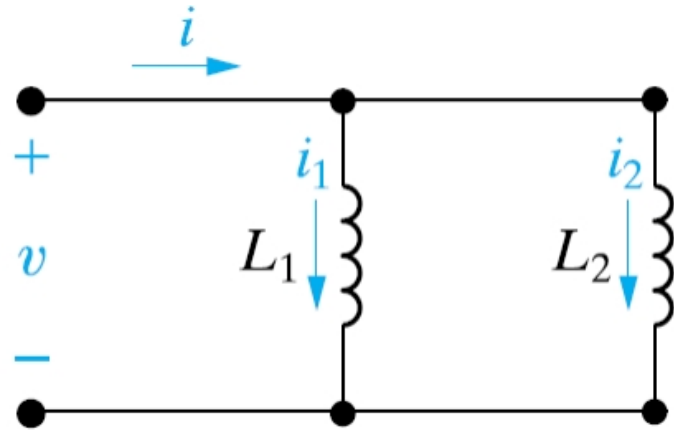

$$(1) L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

$$(2) i_1 = \frac{L_2}{L_1 + L_2} i$$


$$(3) L_1 i_1 = L_2 i_2$$

Assume that $L_1 = 3$ [mH], $L_2 = 2$ [mH], $i = 10$ [A], find i_1 in the given circuit.


$$i_1 = \frac{2}{3 + 2} \times 10 = 4 \text{ [A]}$$

Capacitors in Series and Parallel

Capacitors in series

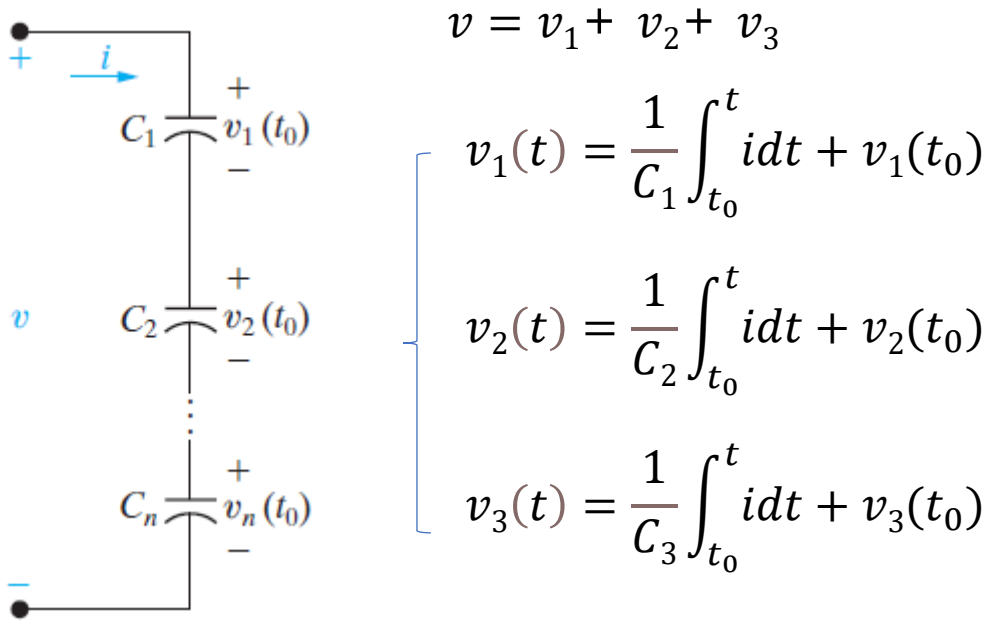

Combining Capacitors in series

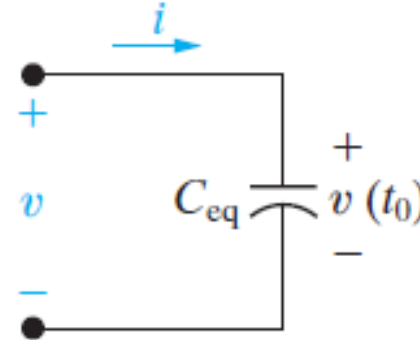

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$


$$v(t_0) = v_1(t_0) + v_2(t_0) + \dots + v_n(t_0)$$

$$\frac{1}{C_{eq}} = \sum_{i=1}^n \frac{1}{C_i}$$

$$v(t_0) = \sum_{j=1}^n v_j(t_0)$$

Capacitors in Series and Parallel


Capacitors in parallel

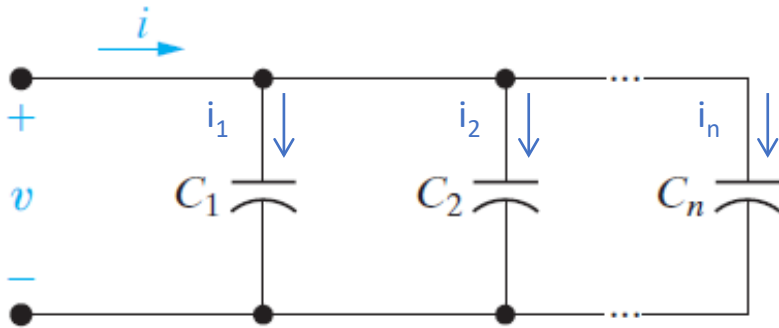

$$i = i_1 + i_2 + i_3$$

$$i_1 = C_1 \frac{dv}{dt} \quad i_2 = C_2 \frac{dv}{dt} \quad i_3 = C_3 \frac{dv}{dt}$$


Combining Capacitors in parallel

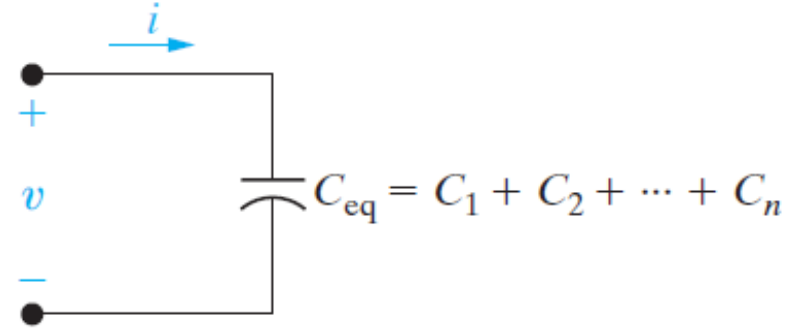

$$C_{eq} = \sum_{i=1}^n C_i$$

Capacitors in Series and Parallel

Example

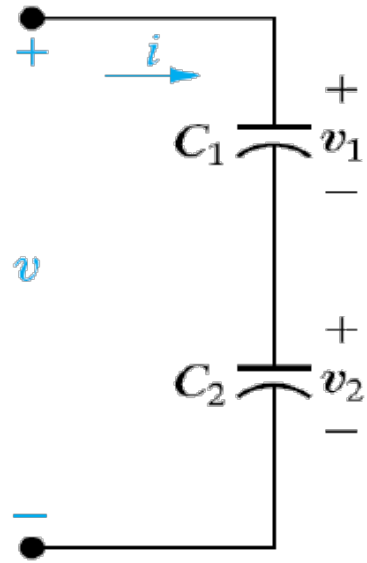

$$(1) C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$(2) v_1 = \frac{C_2}{C_1 + C_2} v$$

$$(3) C_1 v_1 = C_2 v_2$$

$$(4) Q_1 = Q_2$$


Assume that $C_1 = 3 [\mu\text{F}]$, $C_2 = 2 [\mu\text{F}]$, $V_1 = 10 [\text{V}]$, find V_2 and V in the given circuit.

$$v_2 = \frac{C_1}{C_2} v_1 = \frac{3}{2} \times 10 = 15 [\text{V}]$$

$$v = v_1 + v_2 = 10 + 15 = 25 [\text{V}]$$

Capacitors in Series and Parallel

Example

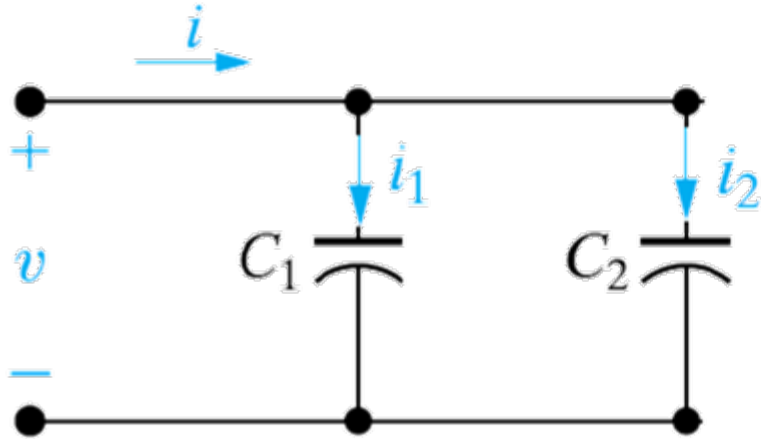

$$(1) C_{eq} = C_1 + C_2$$

$$(2) i_1 = \frac{C_1}{C_1 + C_2} i$$

$$(3) C_1 i_2 = C_2 i_1$$


Assume that $C_1 = 3 [\mu\text{F}]$, $C_2 = 2 [\mu\text{F}]$, $i_1 = 6[\text{A}]$, find i in the given circuit.

$$i = \frac{C_1 + C_2}{C_1} i_1 = \frac{3 + 2}{3} \times 6 = 10 [\text{A}]$$

Example 6.6

Q. Find the equivalent inductance, L_{eq} .


Find the initial current in the equivalent inductor.

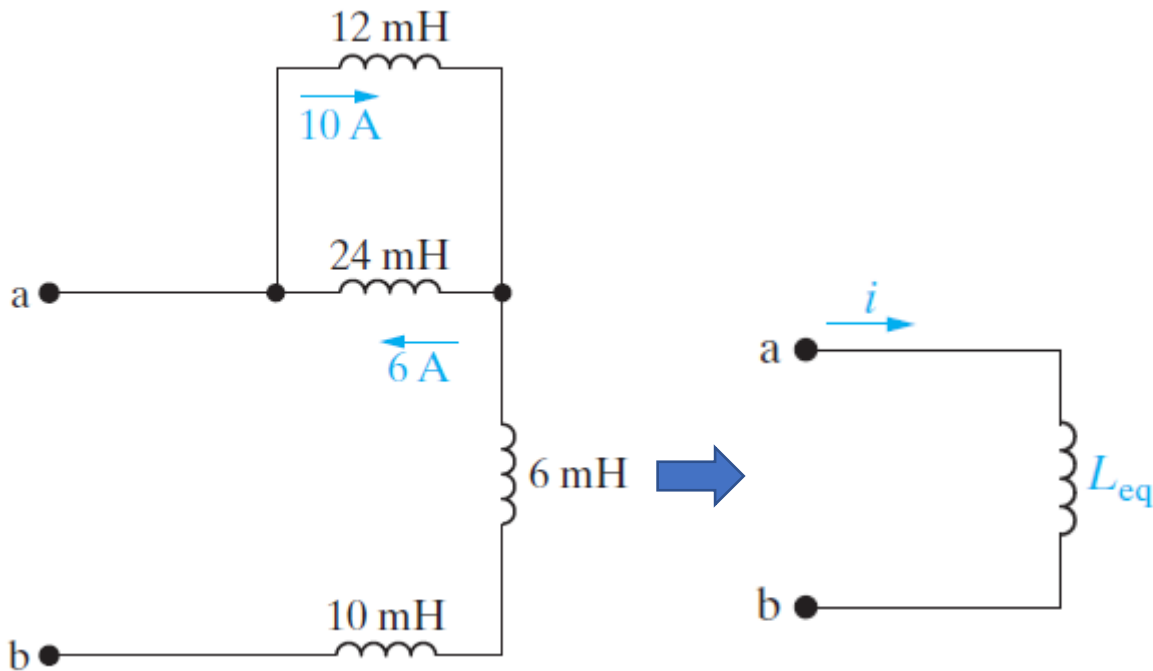

Example 6.6

Q. Find the equivalent inductance, L_{eq} .


Find the initial current in the equivalent inductor.

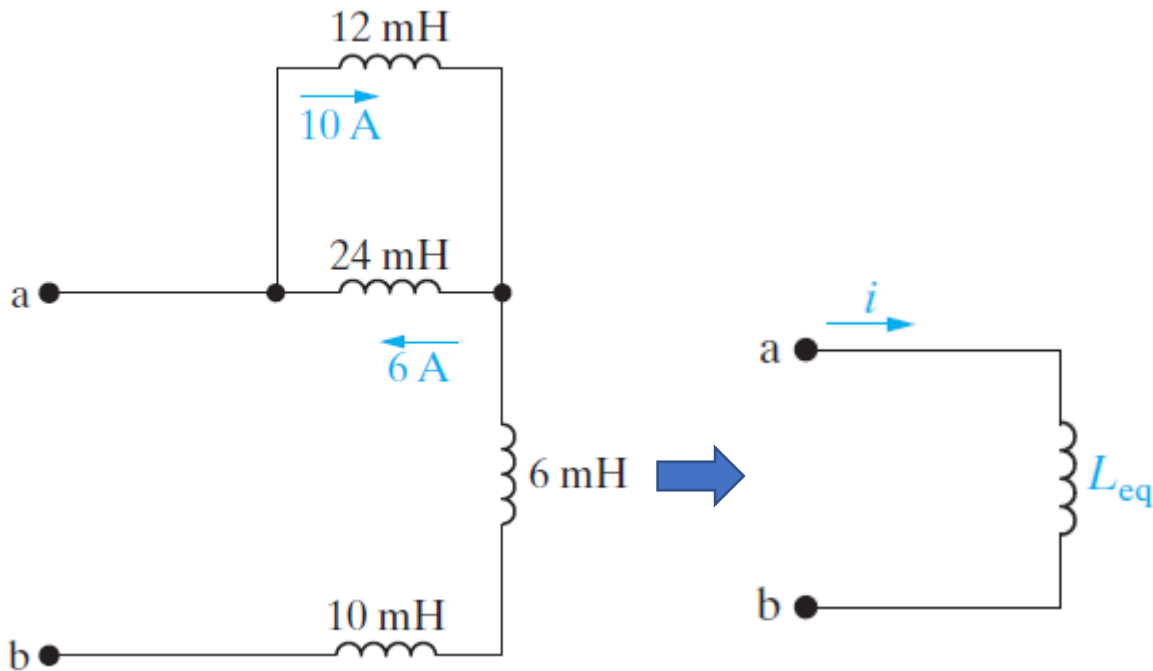

Example 6.7

Q. Find the equivalent Capacitance, C_{eq} .


Find the initial voltage across the equivalent capacitor.

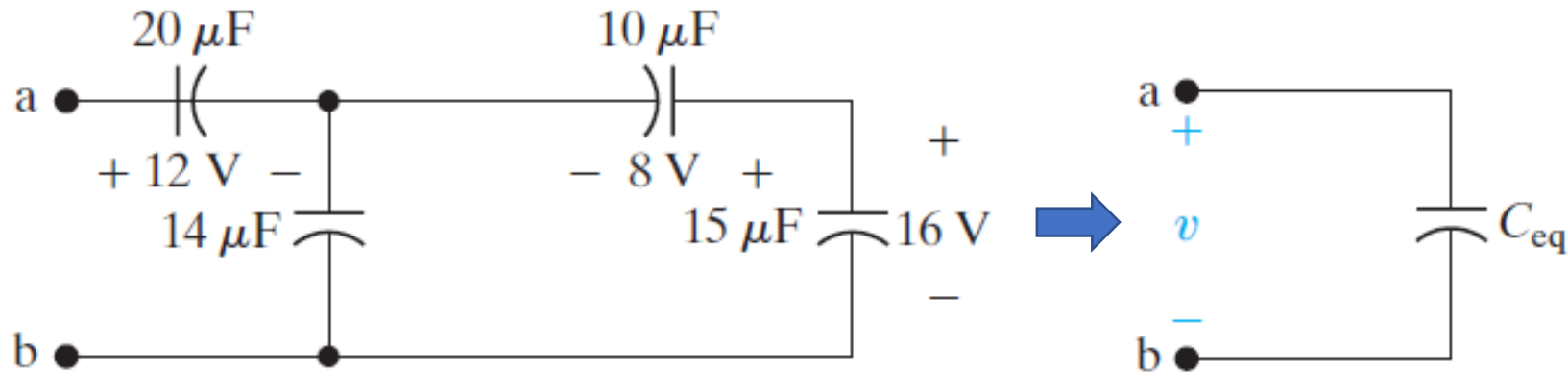

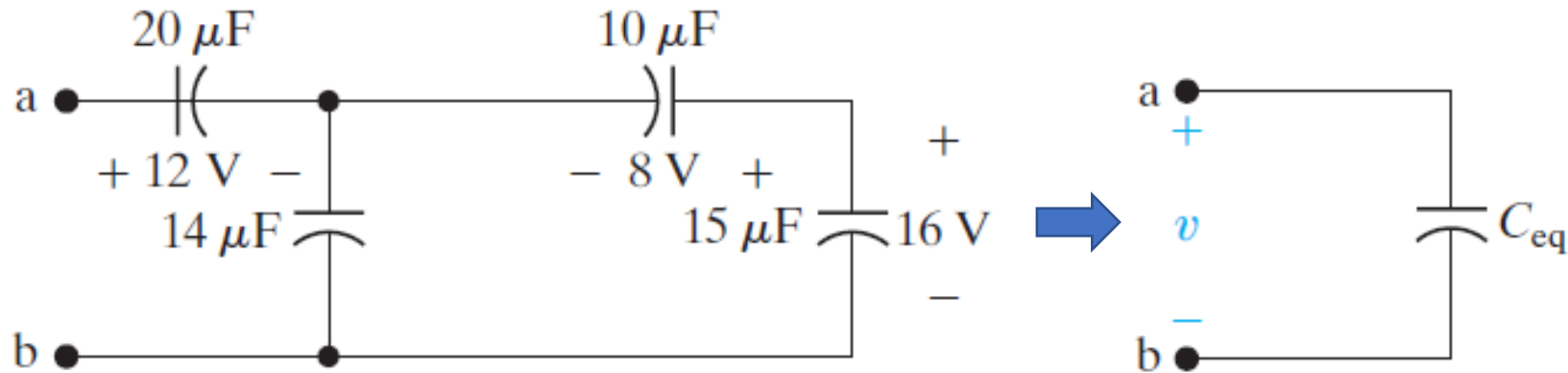Example 6.7

Q. Find the equivalent Capacitance, C_{eq} .

Find the initial voltage across the equivalent capacitor.



Summary

- Inductor & Capacitor
 - IV equation
 - power and energy
 - Series-Parallel Combinations of Inductance and Capacitance
- >> Summarized in [Table 6.1](#)

Table 6.1

	Inductors	Capacitors
Primary v - i equation	$v(t) = L \frac{di(t)}{dt}$	$i(t) = C \frac{dv(t)}{dt}$
Alternate v - i equation	$i(t) = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$	$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$
Initial condition	$i(t_0)$	$v(t_0)$
Behavior with a constant source	If $i(t) = I, v(t) = 0$ and the inductor behaves like a short circuit	If $v(t) = V, i(t) = 0$ and the capacitor behaves like an open circuit
Continuity requirement	$i(t)$ is continuous for all time so $v(t)$ is finite	$v(t)$ is continuous for all time so $i(t)$ is finite
Power equation	$p(t) = v(t)i(t) = Li(t) \frac{di(t)}{dt}$	$p(t) = v(t)i(t) = Cv(t) \frac{dv(t)}{dt}$
Energy equation	$w(t) = \frac{1}{2} Li(t)^2$	$w(t) = \frac{1}{2} Cv(t)^2$
Series-connected equivalent	$L_{eq} = \sum_{j=1}^n L_j$ $i_{eq}(t_0) = i_j(t_0) \quad \text{for all } j$	$\frac{1}{C_{eq}} = \sum_{j=1}^n \frac{1}{C_j}$ $v_{eq}(t_0) = \sum_{j=1}^n v_j(t_0)$
Parallel-connected equivalent	$\frac{1}{L_{eq}} = \sum_{j=1}^n \frac{1}{L_j}$ $i_{eq}(t_0) = \sum_{j=1}^n i_j(t_0)$	$C_{eq} = \sum_{j=1}^n C_j$ $v_{eq}(t_0) = v_j(t_0) \quad \text{for all } j$