


HW#3 posted: 2021/04/07

Submission: 2021/04/16 (Fri) at noon 12:00PM to I-Class.

The solution will be posted on I-Class after class, so the late HW will not be accepted.

You need to submit a scanned pdf (combined) file with reasonable resolution.

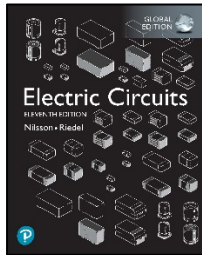Textbook information: Nilsson, Riedel, Electric Circuits, 11th edition, Pearson



Read Chapter 4 of Nilsson's Electric Circuits (11ed) and solve the followings:

[Problem 1] Text page 166, Problem 4.21

[Problem 2] Text page 167, Problem 4.27

[Problem 3] Text page 168, Problem 4.36

[Problem 4] Text page 169, Problem 4.52

[Problem 5] Text page 170, Problem 4.57

[Problem 6] Text page 170, Problem 4.58

[Problem 7] Text page 171, Problem 4.62

[Problem 8] Text page 172, Problem 4.74

[Problem 9] Text page 172, Problem 4.75

[Problem 10] Text page 175, Problem 4.95