
Engineering Circuits Analysis (ICE2002)

Chapter 8. Natural and Step Responses of RLC Circuits – Part 1/2/3/4


Contents

- Introduction to the Natural Response of a Parallel RLC Circuit
- The Forms of the Natural Response of a Parallel RLC Circuit
- The Step Response of a Parallel RLC Circuit
- The Natural and Step Response of a Series RLC Circuit


In Chapter 8

- We discuss the **natural response** and **step response** of circuits containing a **resistor (R)**, an **inductor (L)**, and a **capacitor (C)**, known as **RLC circuits**.
- **Parallel RLC Circuits**: find the voltage across the parallel branches created by the release of energy stored in the inductor or capacitor , or both.
- **Series RLC Circuits**: find the current generated in the series-connected elements by the release of stored energy in the inductor, capacitor, or both.


In Chapter 8

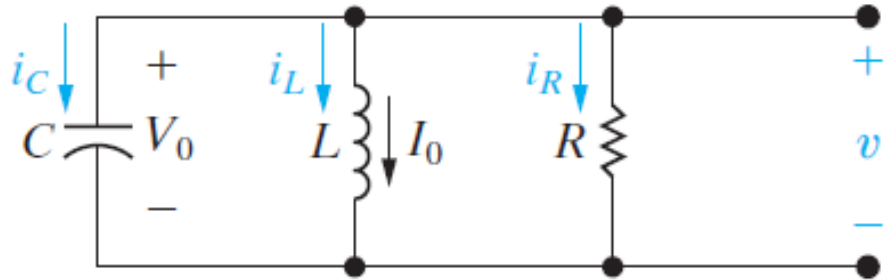

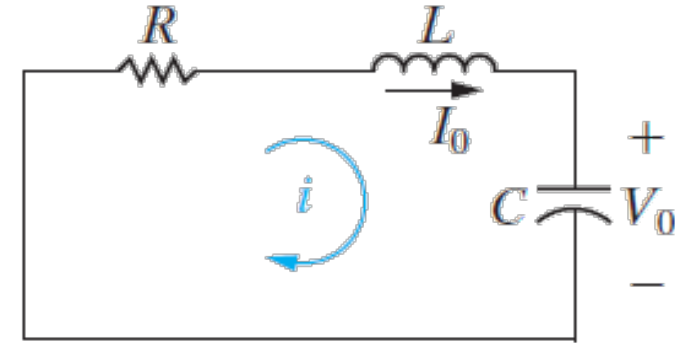
Natural response
of a **parallel** RLC circuit



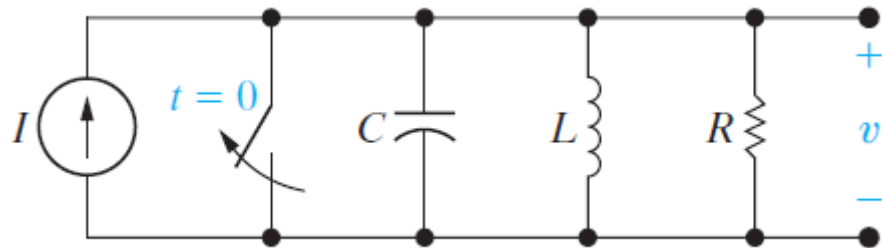Natural response
of a **series** RLC circuit



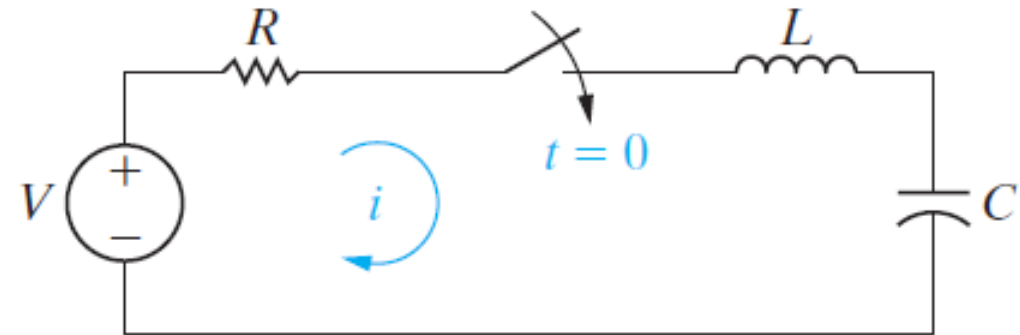Step response
of a **parallel** RLC circuit




Step response
of a **series** RLC circuit

In Chapter 8

	Inductors	Capacitors
Primary v - i equation	$v(t) = L \frac{di(t)}{dt}$	$i(t) = C \frac{dv(t)}{dt}$
Alternate v - i equation	$i(t) = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$	$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$
Initial condition	$i(t_0)$	$v(t_0)$
Behavior with a constant source	If $i(t) = I, v(t) = 0$ and the inductor behaves like a short circuit	If $v(t) = V, i(t) = 0$ and the capacitor behaves like an open circuit
Continuity requirement	$i(t)$ is continuous for all time so $v(t)$ is finite	$v(t)$ is continuous for all time so $i(t)$ is finite
Power equation	$p(t) = v(t)i(t) = Li(t) \frac{di(t)}{dt}$	$p(t) = v(t)i(t) = Cv(t) \frac{dv(t)}{dt}$
Energy equation	$w(t) = \frac{1}{2} Li(t)^2$	$w(t) = \frac{1}{2} Cv(t)^2$
Series-connected equivalent	$L_{eq} = \sum_{j=1}^n L_j$ $i_{eq}(t_0) = i_j(t_0) \quad \text{for all } j$	$\frac{1}{C_{eq}} = \sum_{j=1}^n \frac{1}{C_j}$ $v_{eq}(t_0) = \sum_{j=1}^n v_j(t_0)$
Parallel-connected equivalent	$\frac{1}{L_{eq}} = \sum_{j=1}^n \frac{1}{L_j}$ $i_{eq}(t_0) = \sum_{j=1}^n i_j(t_0)$	$C_{eq} = \sum_{j=1}^n C_j$ $v_{eq}(t_0) = v_j(t_0) \quad \text{for all } j$

Table 6.1

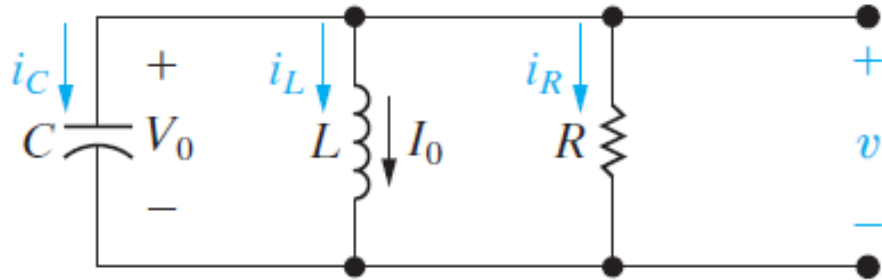Introduction to Natural Response of Parallel RLC Circuit



Natural response
of a parallel RLC circuit

$$i_R + i_L + i_C = 0$$

$$\frac{v}{R} + \frac{1}{L} \int_0^t v d\tau + I_0 + C \frac{dv}{dt} = 0$$

$$\frac{1}{R} \frac{dv}{dt} + \frac{v}{L} + C \frac{d^2v}{dt^2} = 0$$

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$

Ordinary second order differential equation
with constant coefficients

Introduction to Natural Response of Parallel RLC Circuit

General Solution of the Second Order Differential Equation (1)

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0 \quad \rightarrow \quad v = v_1 + v_2 = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$v = A e^{st}$$

$$As^2 e^{st} + \frac{As}{RC} e^{st} + \frac{Ae^{st}}{LC} = 0$$

$$Ae^{st} \left(s^2 + \frac{s}{RC} + \frac{1}{LC} \right) = 0$$

$$\because e^{st} \neq 0, A \neq 0$$

$$s^2 + \frac{s}{RC} + \frac{1}{LC} = 0 \quad \text{Characteristic equation}$$

$$s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}, \quad s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

Introduction to Natural Response of Parallel RLC Circuit

General Solution of the Second Order Differential Equation (2)

$$\boxed{\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0} \rightarrow v = v_1 + v_2 = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad (\text{증명})$$

$$\frac{dv}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

$$\frac{d^2v}{dt^2} = A_1 s_1^2 e^{s_1 t} + A_2 s_2^2 e^{s_2 t}$$

$$A_1 e^{s_1 t} \left(s_1^2 + \frac{1}{RC} s_1 + \frac{1}{LC} \right) + A_2 e^{s_2 t} \left(s_2^2 + \frac{1}{RC} s_2 + \frac{1}{LC} \right) = 0$$

$$\boxed{\therefore v = A_1 e^{s_1 t} + A_2 e^{s_2 t}} \quad \text{Solution}$$

Introduction to Natural Response of Parallel RLC Circuit

General Solution of the Second Order Differential Equation (3)

$$s^2 + \frac{s}{RC} + \frac{1}{LC} = 0 \quad \text{Characteristic equation}$$

$$s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}, \quad s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

Neper Frequency (감쇠 주파수)

$$\alpha = \frac{1}{2RC}$$

Resonant Radian Frequency (공진 주파수)

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Unit [rad/s]

Introduction to Natural Response of Parallel RLC Circuit


General Solution of the Second Order Differential Equation (4)

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \quad \alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$\omega_0^2 < \alpha^2$ Voltage response overdamped (과 감쇠)

$\omega_0^2 > \alpha^2$ Voltage response underdamped (부족 감쇠)

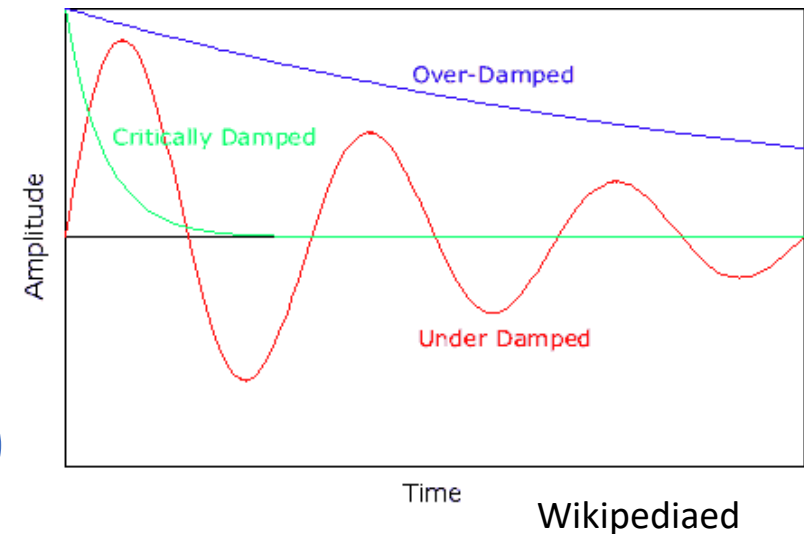
$\omega_0^2 = \alpha^2$ Voltage response critically damped (임계 감쇠)



>> Damping affects the way the voltage response reaches its final (or steady-state) value


Example 8.1

- (a) Find the roots of the characteristic equation, $R=200\Omega$, $L=50\text{mH}$, $C=0.2\mu\text{F}$
- (b) Will the response be overdamped, underdamped, or critically damped?
- (c) Repeat (a) and (b) for $R=312.5\Omega$
- (d) What value of R causes the response to be critically damped?

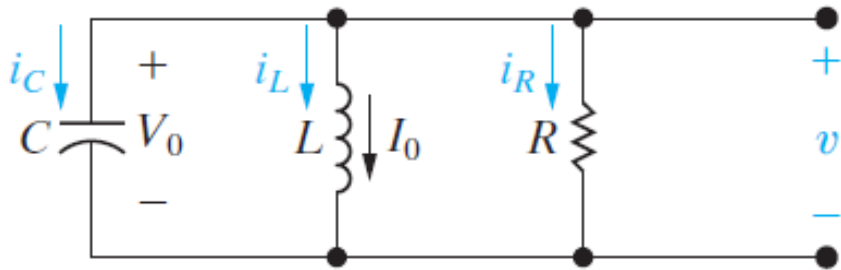

Example 8.1

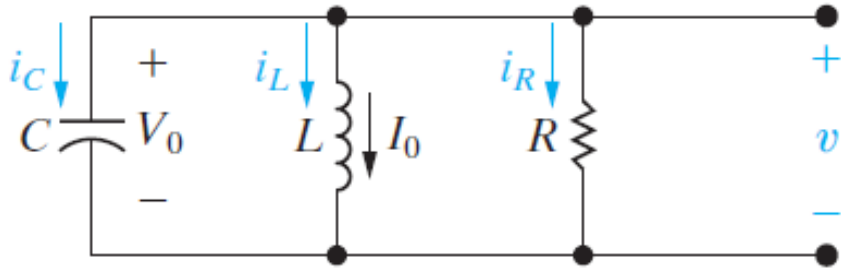- (a) Find the roots of the characteristic equation, $R=200\Omega$, $L=50\text{mH}$, $C=0.2\mu\text{F}$
(b) Will the response be overdamped, underdamped, or critically damped?




$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Example 8.1

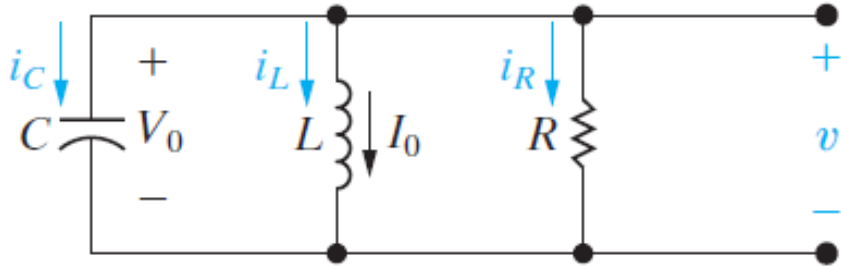(c) Repeat (a) and (b) for $R=312.5\Omega$




$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$


Example 8.1

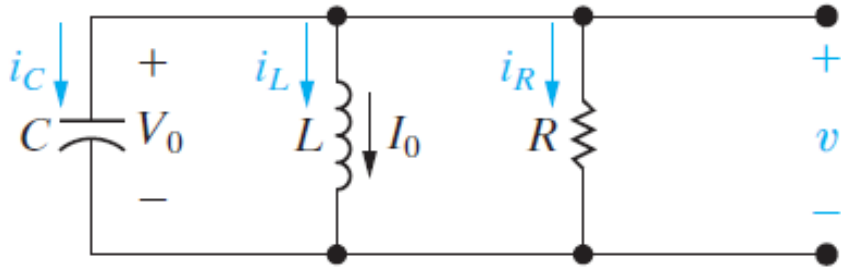(d) What value of R causes the response to be critically damped?



Summary (Part 1)

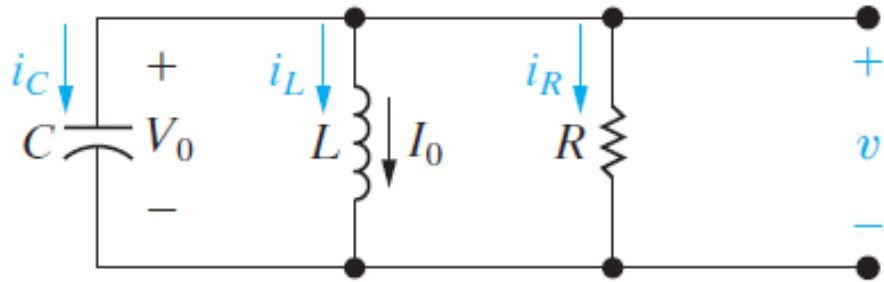■ Natural Response of a Parallel RLC Circuit



Natural response
of a parallel RLC circuit

Parameter	Terminology	Value in Natural Response
s_1, s_2	Characteristic roots	$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$ $s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$
α	Neper frequency	$\alpha = \frac{1}{2RC}$
ω_0	Resonant radian frequency	$\omega_0 = \frac{1}{\sqrt{LC}}$

The Forms of the Natural Response of a Parallel RLC Circuits

(1) $\omega_0^2 < \alpha^2$ Overdamped voltage response (과 감쇠)

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Initial conditions

i) $v(0^+) = A_1 + A_2, \rightarrow v(0^+) = V_0$

ii) $\frac{dv(0^+)}{dt} = s_1 A_1 + s_2 A_2, \rightarrow \frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C}$

$$(i_C(0^+) = -\frac{V_0}{R} - I_0)$$

$$A_1 + A_2 = V_0$$


$$s_1 A_1 + s_2 A_2 + \frac{I_0}{C} + \frac{V_0}{RC} = 0$$

2 equations, 2 unknowns

Example 8.2

$V(0^+) = 12\text{V}$, $i_L(0^+) = 30\text{mA}$

Find the expression for $v(t)$

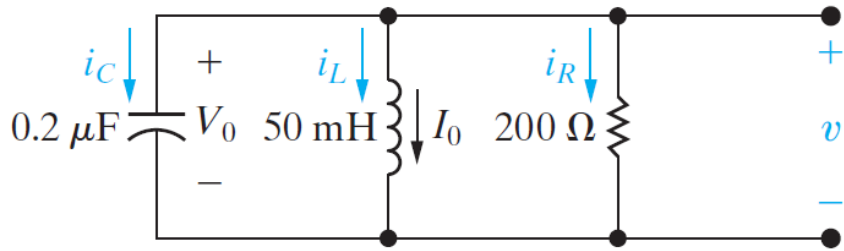

$$v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$


$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Example 8.2

$V(0^+) = 12\text{V}$, $i_L(0^+) = 30\text{mA}$

Find the expression for $v(t)$

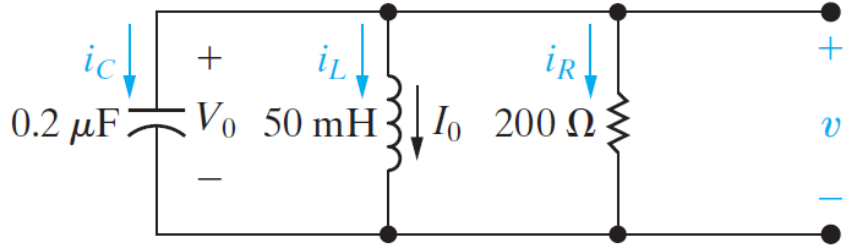


$$v(0^+) = A_1 + A_2, \quad v(0^+) = V_0$$

$$\frac{dv(0^+)}{dt} = s_1 A_1 + s_2 A_2, \quad \frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C}$$

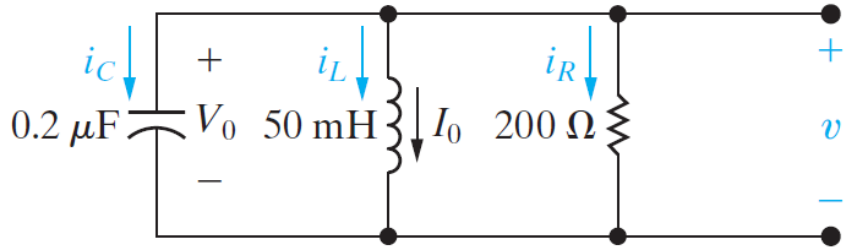
Example 8.2/8.3

$V(0^+) = 12\text{V}$, $i_L(0^+) = 30\text{mA}$

Derive the expression for i_R , i_L , i_C



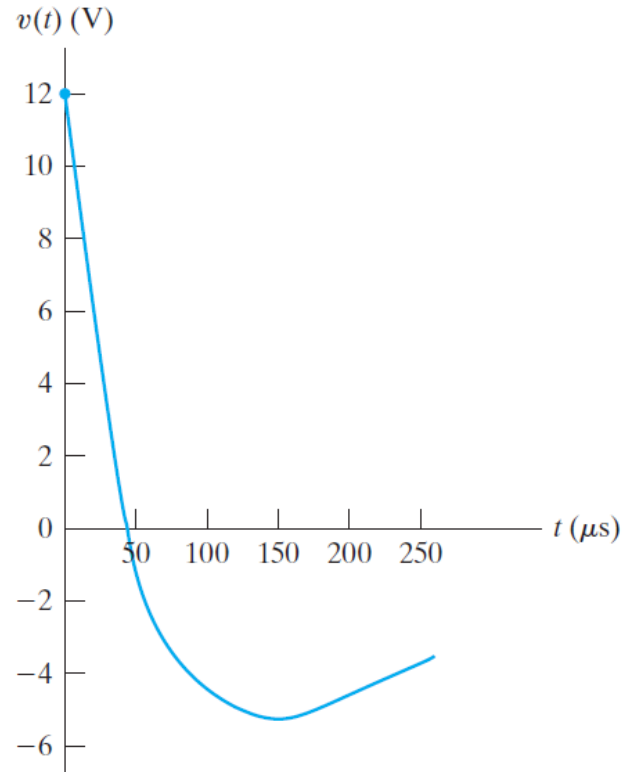The Forms of the Natural Response of a Parallel RLC Circuits



Overdamped
Ex 8.2

The Forms of the Natural Response of a Parallel RLC Circuits

(2) $\omega_0^2 > \alpha^2$ Underdamped voltage response (부족 감쇠)

$$s_1 = -\alpha + \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha + j\sqrt{\omega_0^2 - \alpha^2}$$
$$= -\alpha + j\omega_d$$

$$s_2 = -\alpha - j\omega_d$$

$$v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

ω_d

=Damped Radian Frequency

$$v(t) = A_1 e^{(-\alpha + j\omega_d)t} + A_2 e^{(-\alpha - j\omega_d)t}$$
$$= A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t}$$
$$= e^{-\alpha t} (A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t})$$

Euler's identity: $e^{\pm j\theta} = \cos \theta \pm j \sin \theta$

$$= e^{-\alpha t} (A_1 \cos \omega_d t + jA_1 \sin \omega_d t$$
$$+ A_2 \cos \omega_d t - jA_2 \sin \omega_d t)$$
$$= e^{-\alpha t} [(A_1 + A_2) \cos \omega_d t + j(A_1 - A_2) \sin \omega_d t]$$

The Forms of the Natural Response of a Parallel RLC Circuits

(2) $\omega_0^2 > \alpha^2$ Underdamped voltage response (부족 감쇠)

$$B_1 = A_1 + A_2, \quad B_2 = j(A_1 - A_2)$$

$$v(t) = e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$

Damped Radian Frequency

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$v(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

Initial conditions

i) $v(0^+) = V_0 = B_1$


ii) $\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = -\alpha B_1 + \omega_d B_2$

} 2 equations, 2 unknowns

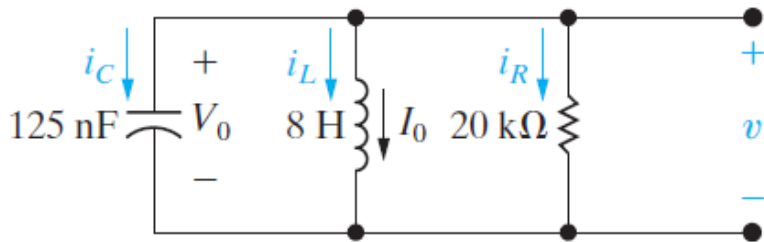Example 8.4

$$V_0=0, I_0=-12.25 \text{ mA}$$

Calculate the voltage response $t \geq 0$



$$v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_1 = -\alpha + \sqrt{-(\omega_0^2 - \alpha^2)} = -\alpha + j\sqrt{\omega_0^2 - \alpha^2}$$
$$= -\alpha + j\omega_d$$

$$s_2 = -\alpha - j\omega_d$$


$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$v(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

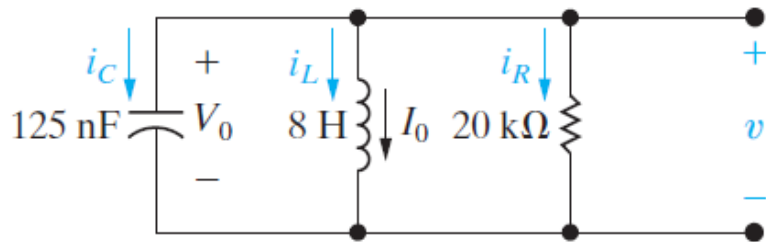Example 8.4

$$V_0 = 0, I_0 = -12.25 \text{ mA}$$


Calculate the voltage response $t \geq 0$




$$v(0^+) = V_0 = B_1$$

$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = -\alpha B_1 + \omega_d B_2$$

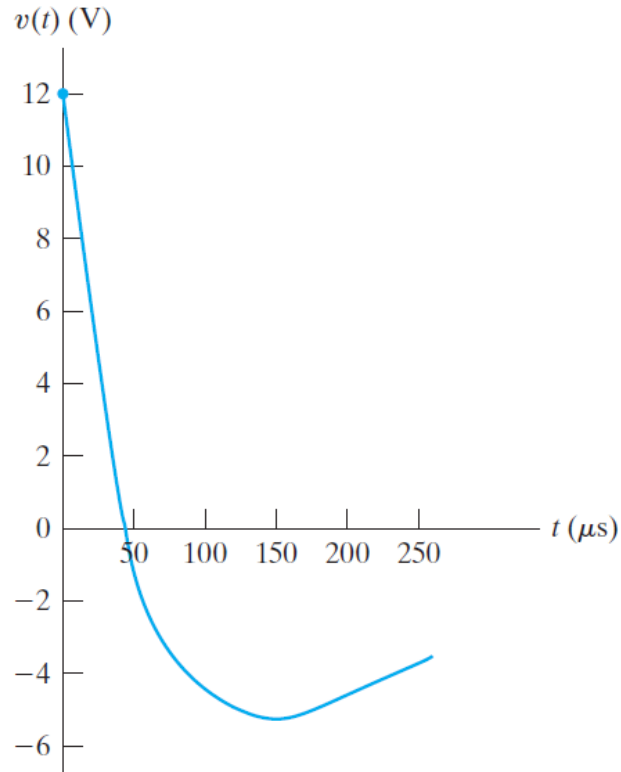The Forms of the Natural Response of a Parallel RLC Circuits



Overdamped
Ex 8.2

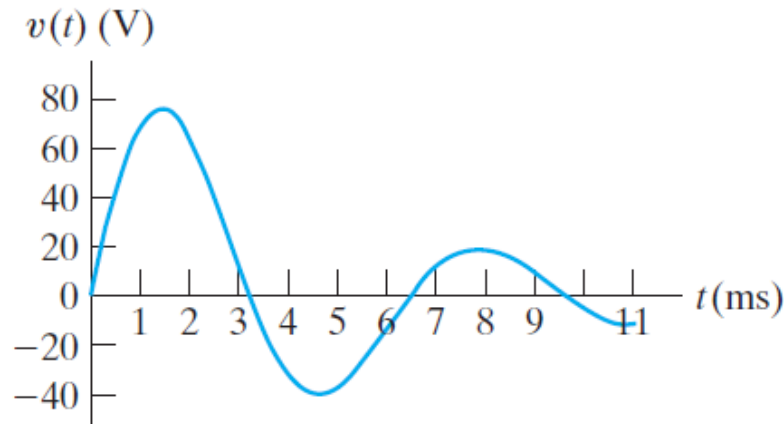

Underdamped
Ex 8.4

The Forms of the Natural Response of a Parallel RLC Circuits

(3) $\omega_0^2 = \alpha^2$ Critically damped voltage response (임계 감쇠)

$$s_1 = s_2 = -\alpha = -\frac{1}{2RC}$$

$$v_1 = D_1 t e^{st}, v_2 = D_2 e^{st}$$

$$v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

Initial conditions

i) $v(0^+) = V_0 = D_2$


ii) $\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = D_1 - \alpha D_2$

} 2 equations, 2 unknowns



Example 8.5

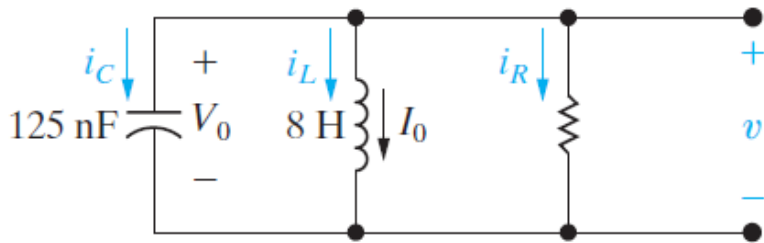- (a) Find the value of R that results in a critically damped voltage response
- (b) Calculate $v(t)$ for $t \geq 0$




$$s_1 = s_2 = -\alpha = -\frac{1}{2RC}$$

$$v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$


$$v(0^+) = V_0 = D_2$$

$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C} = D_1 - \alpha D_2$$

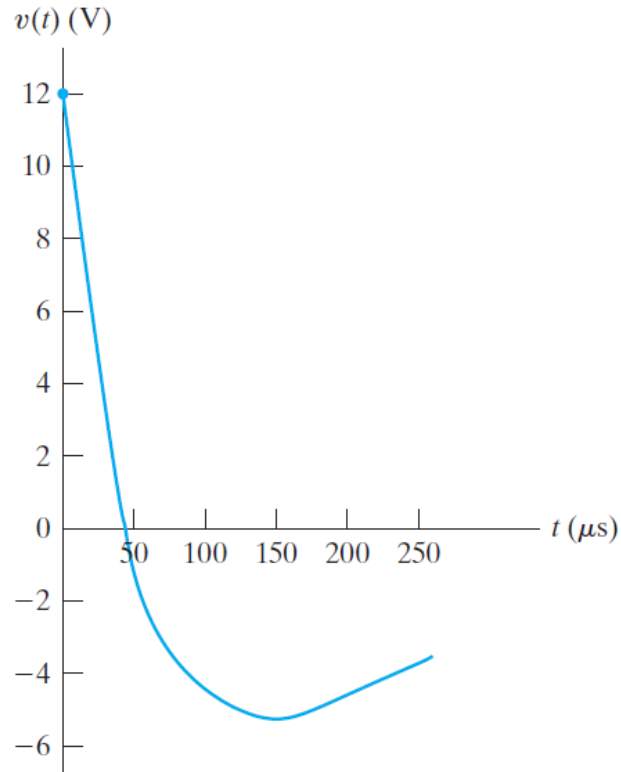
The Forms of the Natural Response of a Parallel RLC Circuits



Overdamped
Ex 8.2

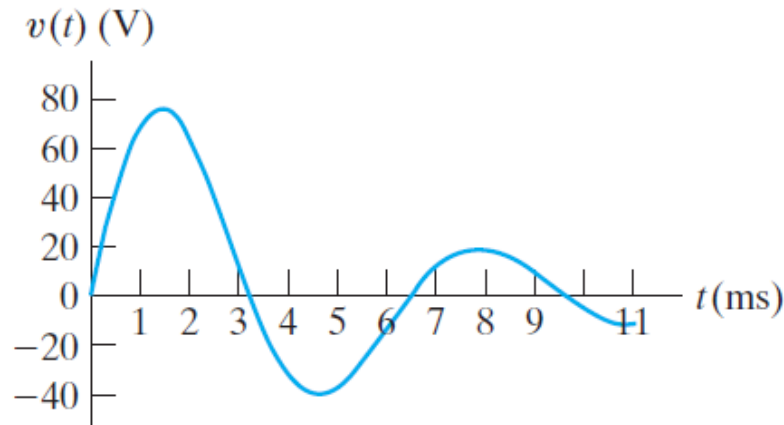


Underdamped
Ex 8.4

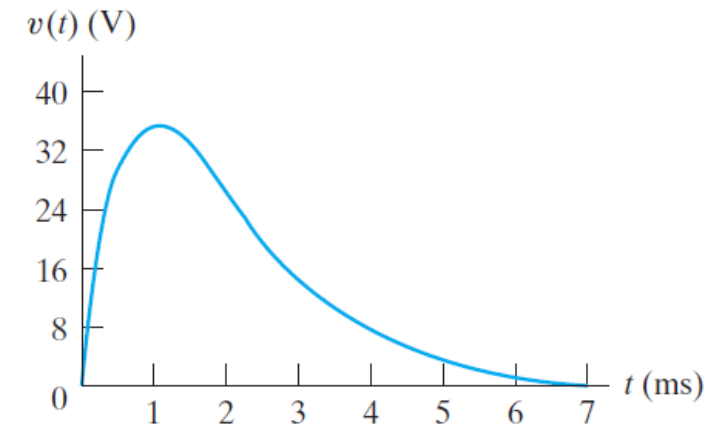

Critically damped
Ex 8.5

Summary (Part 2)

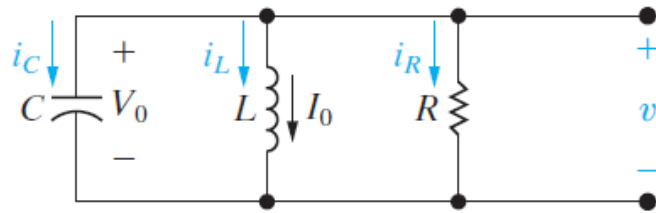■ Natural Response of a Parallel RLC Circuit



Characteristic equation

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$

Neper, resonant, and damped frequencies

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \sqrt{\frac{1}{LC}} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

Roots of the characteristic equation

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$\alpha^2 > \omega_0^2$: overdamped

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}, \quad t \geq 0$$

$$v(0^+) = A_1 + A_2 = V_0$$

$$\frac{dv(0^+)}{dt} = s_1 A_1 + s_2 A_2 = \frac{1}{C} \left(\frac{-V_0}{R} - I_0 \right)$$

$\alpha^2 < \omega_0^2$: underdamped

$$v(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t, \quad t \geq 0$$

$$v(0^+) = B_1 = V_0$$

$$\frac{dv(0^+)}{dt} = -\alpha B_1 + \omega_d B_2 = \frac{1}{C} \left(\frac{-V_0}{R} - I_0 \right)$$

$\alpha^2 = \omega_0^2$: critically damped


$$v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}, \quad t \geq 0$$

$$v(0^+) = D_2 = V_0$$


$$\frac{dv(0^+)}{dt} = D_1 - \alpha D_2 = \frac{1}{C} \left(\frac{-V_0}{R} - I_0 \right)$$

Table 8.2

Step Response of a Parallel RLC Circuit

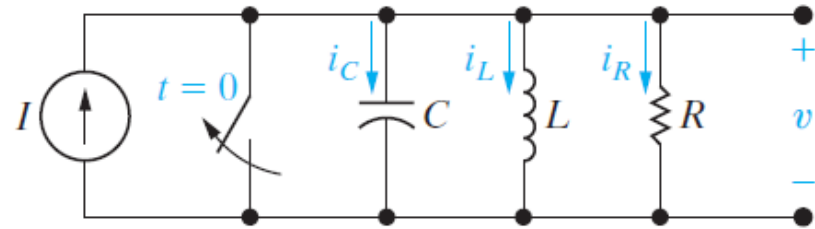

$t \rightarrow \infty$

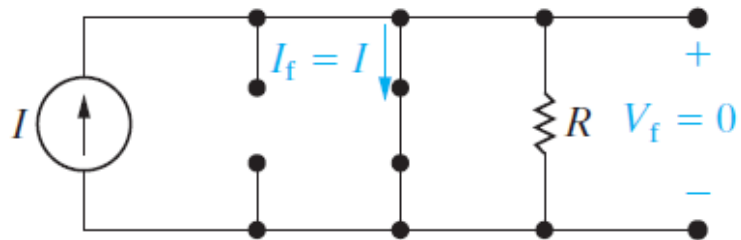

Step response
of a parallel RLC circuit

$$i_L + i_R + i_C = I$$

$$i_L + \frac{v}{R} + C \frac{dv}{dt} = I \quad v = L \frac{di_L}{dt}, \frac{dv}{dt} = L \frac{d^2 i_L}{dt^2}$$

$$i_L + \frac{L}{R} \frac{di_L}{dt} + LC \frac{d^2 i_L}{dt^2} = I$$

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{I}{LC}$$

Ordinary second order differential equation
with constant coefficients

Step Response of a Parallel RLC Circuit

i) Indirect approach

$$i_L + \frac{v}{R} + C \frac{dv}{dt} = I$$

$$\frac{1}{L} \int_0^t v d\tau + \frac{v}{R} + C \frac{dv}{dt} = I$$

$$\frac{v}{L} + \frac{1}{R} \frac{dv}{dt} + C \frac{d^2v}{dt^2} = 0$$

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$

- $v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$
- $v = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$
- $v = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$

Note:

$$C \frac{dv}{dt} + i_L + \frac{v}{R} = I$$

$$i_L = I - C \frac{dv}{dt} - \frac{v}{R}$$

Step Response of a Parallel RLC Circuit

i) Indirect approach

$$i_L + \frac{v}{R} + C \frac{dv}{dt} = I$$

$$\frac{1}{L} \int_0^t v d\tau + \frac{v}{R} + C \frac{dv}{dt} = I$$

$$\frac{v}{L} + \frac{1}{R} \frac{dv}{dt} + C \frac{d^2v}{dt^2} = 0$$

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$

Note:

$$C \frac{dv}{dt} + i_L + \frac{v}{R} = I$$

$$i_L = I - C \frac{dv}{dt} - \frac{v}{R}$$

- $v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$
- $v = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$
- $v = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$
- $i_L = I + A_1' e^{s_1 t} + A_2' e^{s_2 t}$
- $i_L = I + B_1' e^{-\alpha t} \cos \omega_d t + B_2' e^{-\alpha t} \sin \omega_d t$
- $i_L = I + D_1' t e^{-\alpha t} + D_2' e^{-\alpha t}$

Step Response of a Parallel RLC Circuit

ii) Direct approach

$$\frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{I}{LC}$$


$I = I_f + (\text{function of the same form as the natural response})$

$V = V_f + (\text{function of the same form as the natural response})$

Example 8.6

DC current source of 24 mA is applied. The value of the resistor is $R=400\Omega$.

Find i_L for $t \geq 0$.

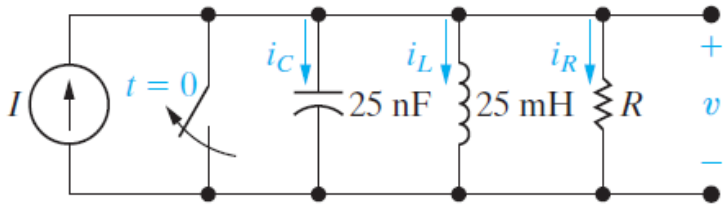


$$\alpha = \frac{1}{2RC} \quad \omega_0 = \sqrt{\frac{1}{LC}} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

- $i_L = I + A_1' e^{s_1 t} + A_2' e^{s_2 t}$
- $i_L = I + B_1' e^{-\alpha t} \cos \omega_d t + B_2' e^{-\alpha t} \sin \omega_d t$
- $i_L = I + D_1' t e^{-\alpha t} + D_2' e^{-\alpha t}$

Example 8.7

DC current source of 24 mA is applied. The value of the resistor is $R=625\Omega$.

Find i_L for $t \geq 0$.

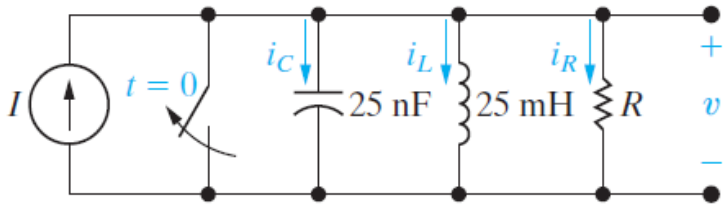


$$\alpha = \frac{1}{2RC} \quad \omega_0 = \sqrt{\frac{1}{LC}} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

- $i_L = I + A_1' e^{s_1 t} + A_2' e^{s_2 t}$
- $i_L = I + B_1' e^{-\alpha t} \cos \omega_d t + B_2' e^{-\alpha t} \sin \omega_d t$
- $i_L = I + D_1' t e^{-\alpha t} + D_2' e^{-\alpha t}$

Example 8.8

DC current source of 24 mA is applied. The value of the resistor is $R=500\Omega$.

Find i_L for $t \geq 0$.


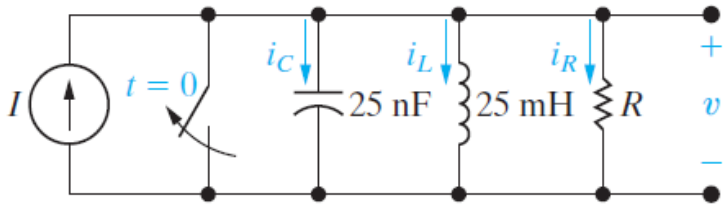


$$\alpha = \frac{1}{2RC} \quad \omega_0 = \sqrt{\frac{1}{LC}} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

- $i_L = I + A_1' e^{s_1 t} + A_2' e^{s_2 t}$
- $i_L = I + B_1' e^{-\alpha t} \cos \omega_d t + B_2' e^{-\alpha t} \sin \omega_d t$
- $i_L = I + D_1' t e^{-\alpha t} + D_2' e^{-\alpha t}$

Example 8.9

Example 8.6, 8.7, and 8.8

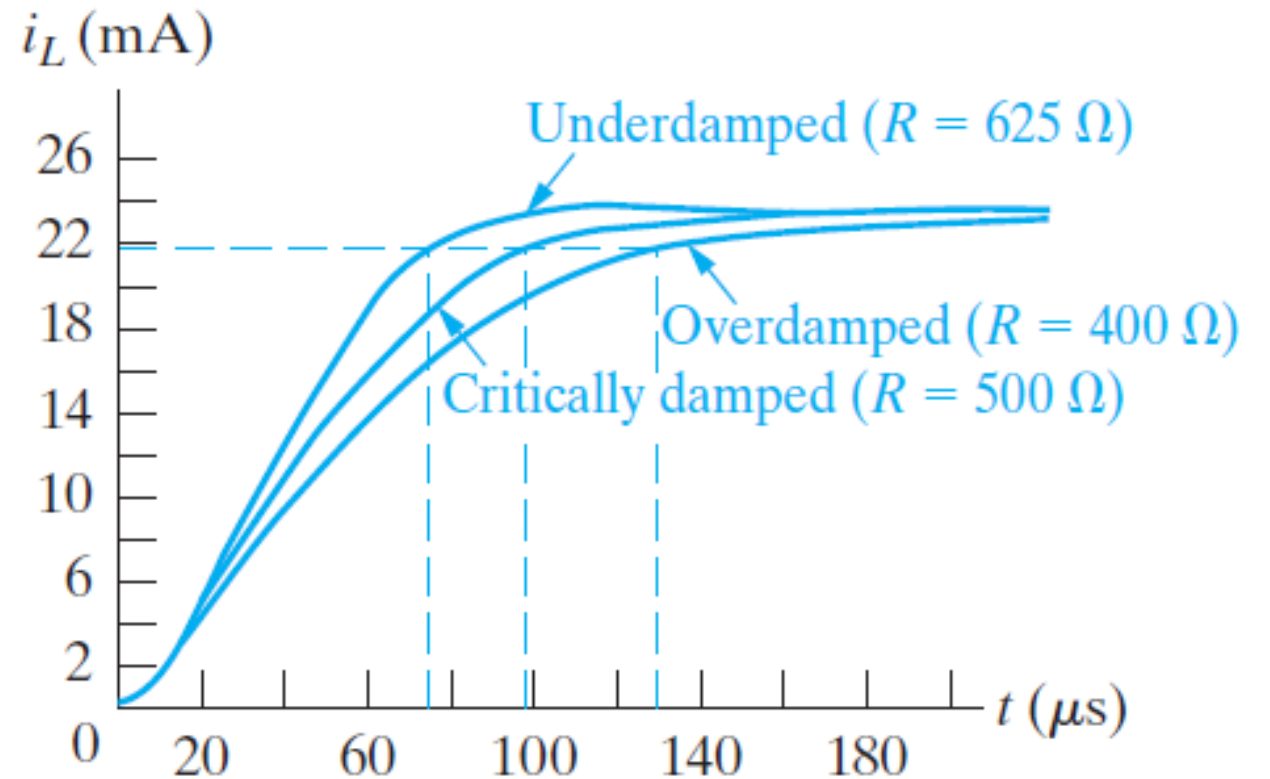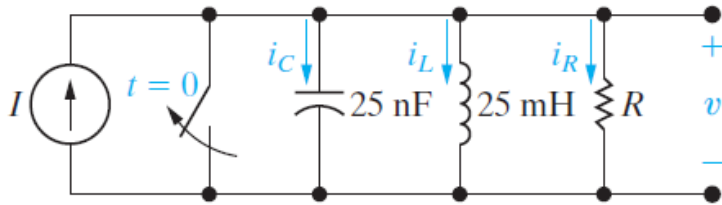

Summary


- Natural Response of a Parallel RLC Circuit
- Step Response of a Parallel RLC Circuit

$$I = I_f + (\text{function of the same form as the natural response})$$

$$V = V_f + (\text{function of the same form as the natural response})$$

Summary (Part 3)

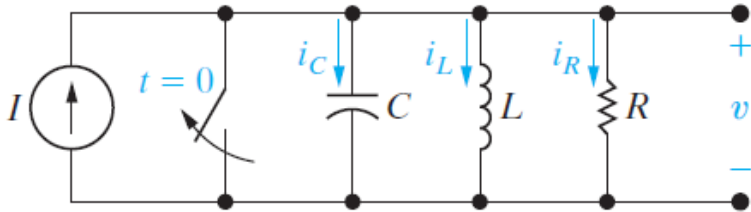■ Step Response of a Parallel RLC Circuit



Characteristic equation

Neper, resonant, and damped frequencies

Roots of the characteristic equation

$\alpha^2 > \omega_0^2$: overdamped

$\alpha^2 < \omega_0^2$: underdamped

$\alpha^2 = \omega_0^2$: critically damped

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = \frac{I}{LC}$$

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \sqrt{\frac{1}{LC}} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$i_L(t) = I_f + A'_1 e^{s_1 t} + A'_2 e^{s_2 t}, \quad t \geq 0$$

$$i_L(0^+) = I_f + A'_1 + A'_2 = I_0$$

$$\frac{di_L(0^+)}{dt} = s_1 A'_1 + s_2 A'_2 = \frac{V_0}{L}$$

$$i_L(t) = I_f + B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t, \quad t \geq 0$$

$$i_L(0^+) = I_f + B'_1 = I_0$$

$$\frac{di_L(0^+)}{dt} = -\alpha B'_1 + \omega_d B'_2 = \frac{V_0}{L}$$


$$i_L(t) = I_f + D'_1 t e^{-\alpha t} + D'_2 e^{-\alpha t}, \quad t \geq 0$$

$$i_L(0^+) = I_f + D'_2 = I_0$$

$$\frac{di_L(0^+)}{dt} = D'_1 - \alpha D'_2 = \frac{V_0}{L}$$

Table 8.3

Natural Response of a Series RLC Circuit

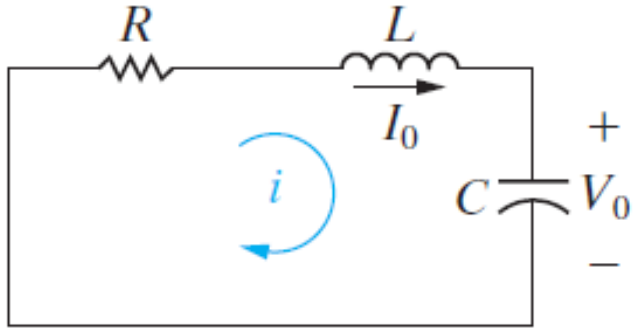

Natural response
of a series RLC circuit

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_0^t i d\tau + V_0 = 0$$


$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C} = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

Ordinary second order differential equation
with constant coefficients


Natural Response of a Series RLC Circuit

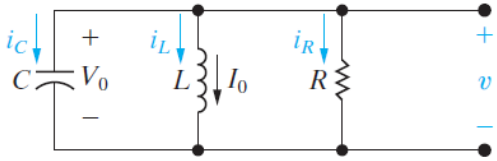Parallel RLC circuit $\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0 \rightarrow s^2 + \frac{s}{RC} + \frac{1}{LC} = 0$



$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \quad \alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

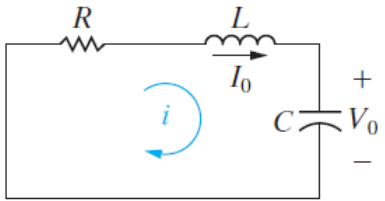Series RLC circuit $\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0 \rightarrow s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$



$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Natural Response of a Series RLC Circuit

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \quad \alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$\omega_0^2 < \alpha^2$ Overdamped voltage response (과 감쇠)

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$


$\omega_0^2 > \alpha^2$ Underdamped voltage response (부족 감쇠)

$$i(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

$\omega_0^2 = \alpha^2$ Critically damped voltage response (임계 감쇠)

$$i(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

Step Response of a Series RLC Circuit

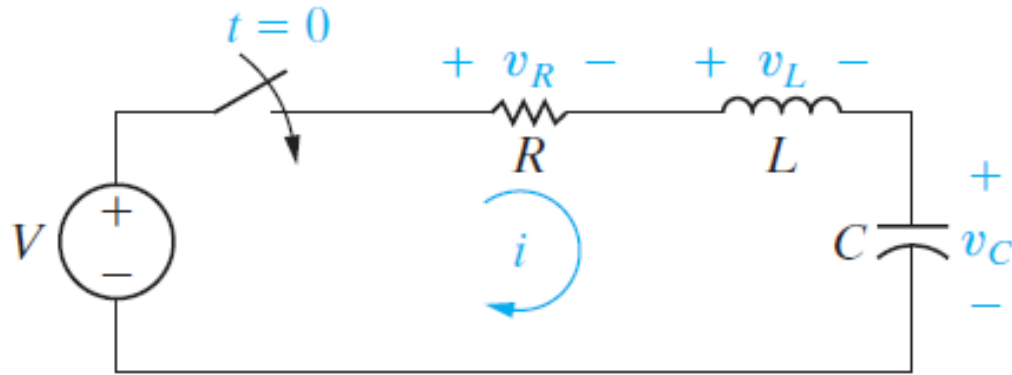

Step response
of a series RLC circuit

$$V = v_R + v_L + v_C$$


$$V = Ri + L \frac{di}{dt} + v_C \quad i = C \frac{dv_C}{dt}, \frac{di}{dt} = C \frac{d^2v_C}{dt^2}$$

$$v_C + RC \frac{dv_C}{dt} + LC \frac{d^2v_C}{dt^2} = V$$

$$\boxed{\frac{d^2v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{v_C}{LC} = \frac{V}{LC}}$$

Ordinary second order differential equation
with constant coefficients

Step Response of a Series RLC Circuit

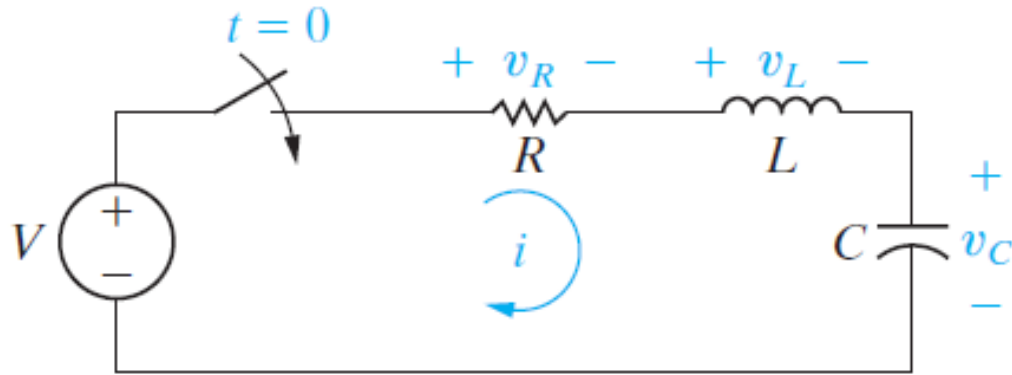

Step response
of a series RLC circuit

$$\frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{v_C}{LC} = \frac{V}{LC}$$


$$v_C = V_f + A_1' e^{s_1 t} + A_2' e^{s_2 t}$$

$$v_C = V_f + B_1' e^{-\alpha t} \cos \omega_d t + B_2' e^{-\alpha t} \sin \omega_d t$$

$$v_C = V_f + D_1' t e^{-\alpha t} + D_2' e^{-\alpha t}$$

Example 8.11

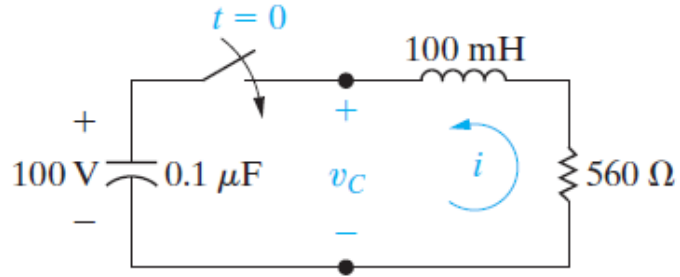(a) Find $i(t)$ for $t \geq 0$ (b) Find $V_c(t)$ for $t \geq 0$.



$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$


$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$i(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

$$i(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$


Example 8.11

(a) Find $i(t)$ for $t \geq 0$ (b) Find $V_c(t)$ for $t \geq 0$.

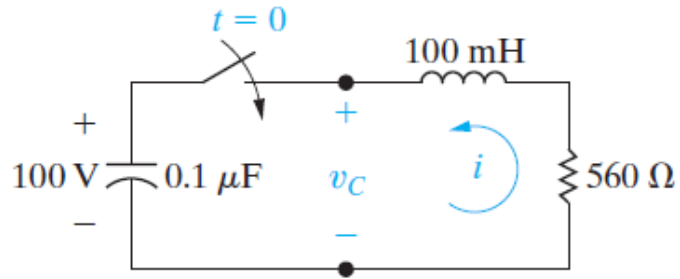

Example 8.12

Find $V_C(t)$ for $t \geq 0$.

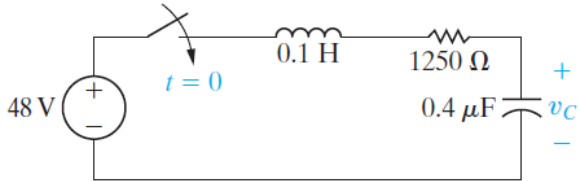

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$


$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$v_C = V_f + A_1' e^{s_1 t} + A_2' e^{s_2 t}$$

$$v_C = V_f + B_1' e^{-\alpha t} \cos \omega_d t + B_2' e^{-\alpha t} \sin \omega_d t$$

$$v_C = V_f + D_1' t e^{-\alpha t} + D_2' e^{-\alpha t}$$

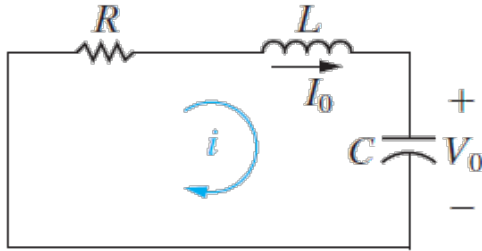Summary (Part 4) Natural response of series RLC Circuit



Characteristic equation

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

Neper, resonant, and damped frequencies

$$\alpha = \frac{R}{2L} \quad \omega_0 = \sqrt{\frac{1}{LC}} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

Roots of the characteristic equation

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$\alpha^2 > \omega_0^2$: overdamped

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}, \quad t \geq 0$$

$$i(0^+) = A_1 + A_2 = I_0$$

$$\frac{di(0^+)}{dt} = s_1 A_1 + s_2 A_2 = \frac{1}{L} (-RI_0 - V_0)$$

$\alpha^2 < \omega_0^2$: underdamped

$$i(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t, \quad t \geq 0$$

$$i(0^+) = B_1 = I_0$$

$$\frac{di(0^+)}{dt} = -\alpha B_1 + \omega_d B_2 = \frac{1}{L} (-RI_0 - V_0)$$

$\alpha^2 = \omega_0^2$: critically damped


$$i(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}, \quad t \geq 0$$

$$i(0^+) = D_2 = I_0$$

$$\frac{di(0^+)}{dt} = D_1 - \alpha D_2 = \frac{1}{L} (-RI_0 - V_0)$$

Table 8.4

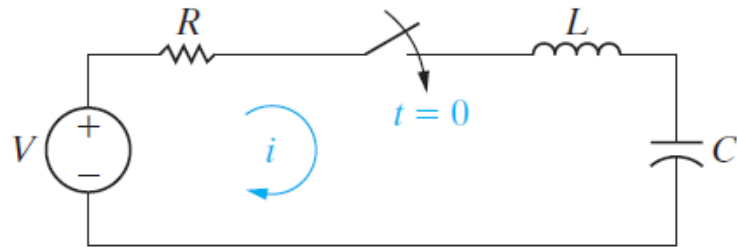Summary (Part 4) Step response of series RLC Circuit



Characteristic equation

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = \frac{V}{LC}$$

Neper, resonant, and damped frequencies

$$\alpha = \frac{R}{2L} \quad \omega_0 = \sqrt{\frac{1}{LC}} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

Roots of the characteristic equation

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$\alpha^2 > \omega_0^2$: overdamped

$$v_C(t) = V_f + A'_1 e^{s_1 t} + A'_2 e^{s_2 t}, t \geq 0$$

$$v_C(0^+) = V_f + A'_1 + A'_2 = V_0$$

$$\frac{dv_C(0^+)}{dt} = s_1 A'_1 + s_2 A'_2 = \frac{I_0}{C}$$

$\alpha^2 < \omega_0^2$: underdamped

$$v_C(t) = V_f + B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t, t \geq 0$$

$$v_C(0^+) = V_f + B'_1 = V_0$$

$$\frac{dv_C(0^+)}{dt} = -\alpha B'_1 + \omega_d B'_2 = \frac{I_0}{C}$$

$\alpha^2 = \omega_0^2$: critically damped

$$v_C(t) = V_f + D'_1 t e^{-\alpha t} + D'_2 e^{-\alpha t}, t \geq 0$$

$$v_C(0^+) = V_f + D'_2 = V_0$$

$$\frac{dv_C(0^+)}{dt} = D'_1 - \alpha D'_2 = \frac{I_0}{C}$$

Table 8.5